
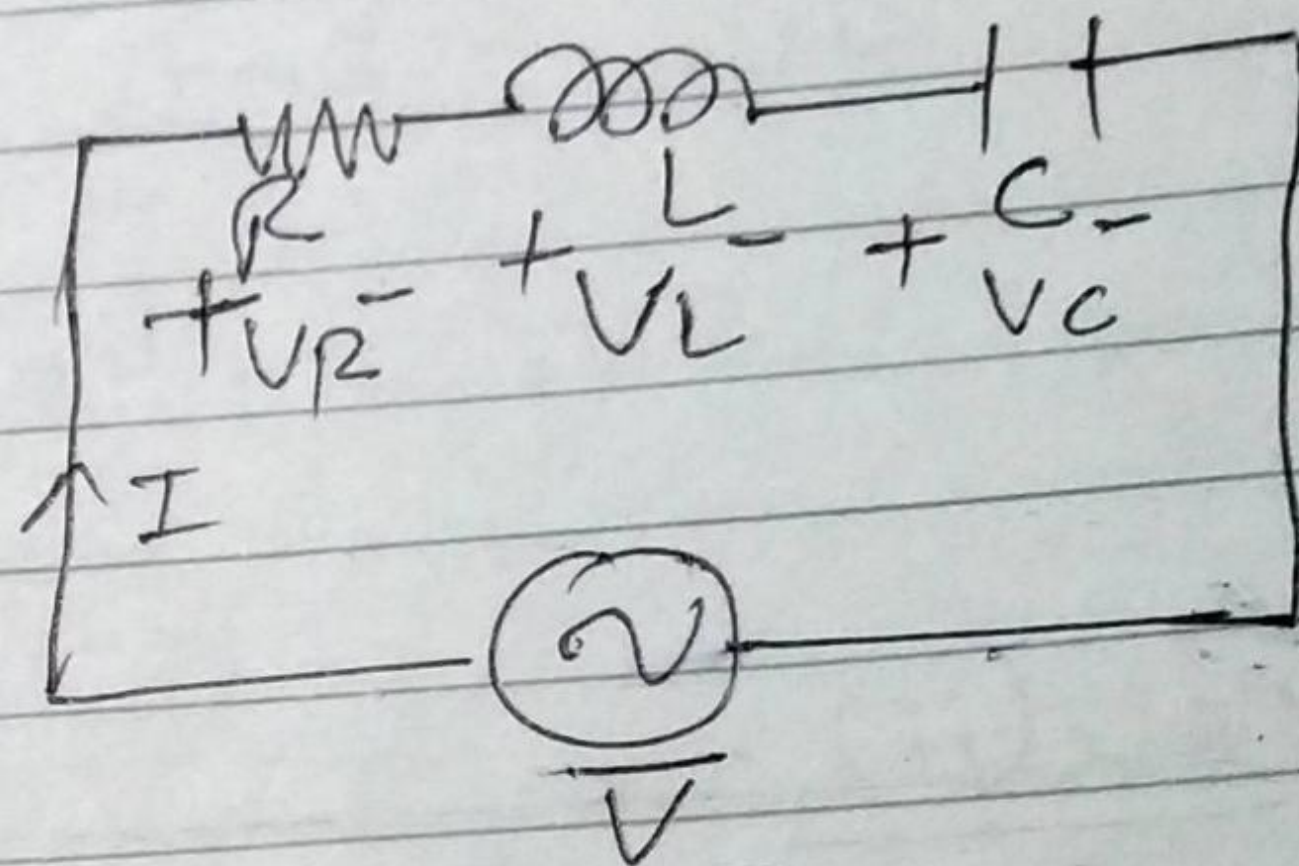


## RESONANCE :-

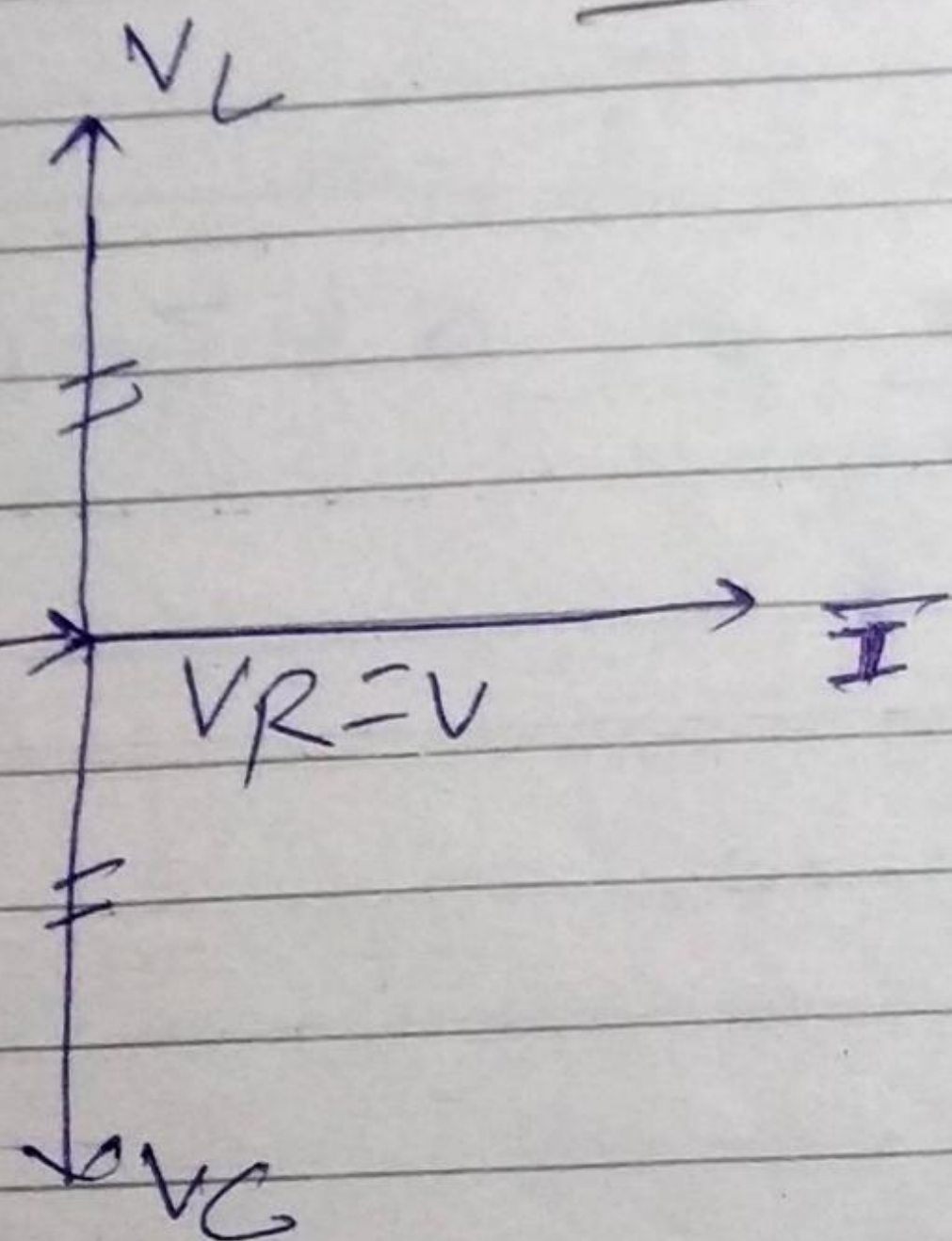

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$

## At Resonance

$$V_L = V_C$$

$$I X_L = I X_C$$

$$X_L = X_C$$

$$\omega_0 L = \frac{1}{\omega_0 C}$$

$$\omega_0^2 = \frac{1}{LC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/sec}$$

$V_L$  and  $V_C$  are equal and opposite so  $V = V_R$

Resonance happens when reactive component is zero.



→ for the occurrence of Resonance in any system two energies are required.


→ In an electrical system these two ~~energies~~ are provided by inductor and capacitor in the form of magnetic and electric field respectively.

→ The Ckt is said to be in Resonance when source Voltage and source current are in phase.

→ The Resonant frequency indicates the rate at which energy transformation takes place b/w the inductor and capacitor.


$$Z = R + j(X_L - X_C) \quad Z = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

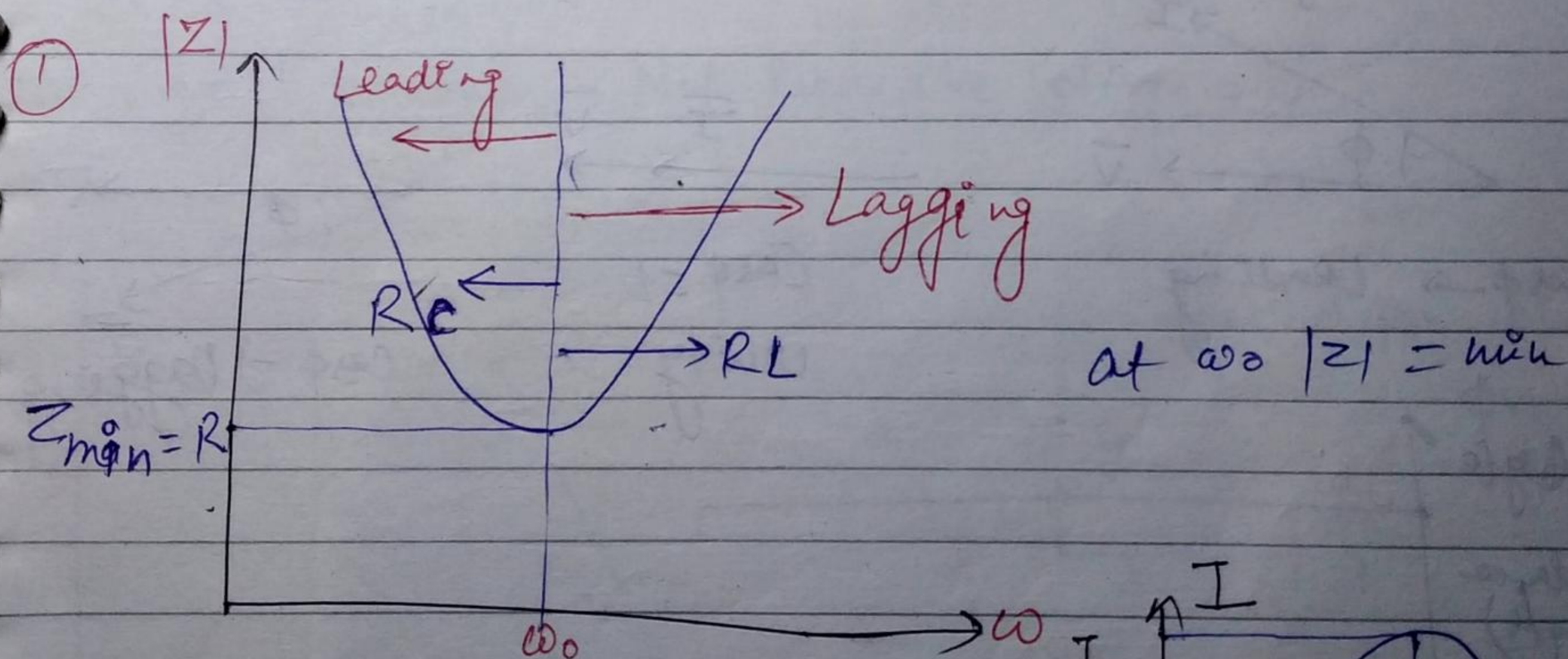

②  $I = \frac{V}{|Z|}$

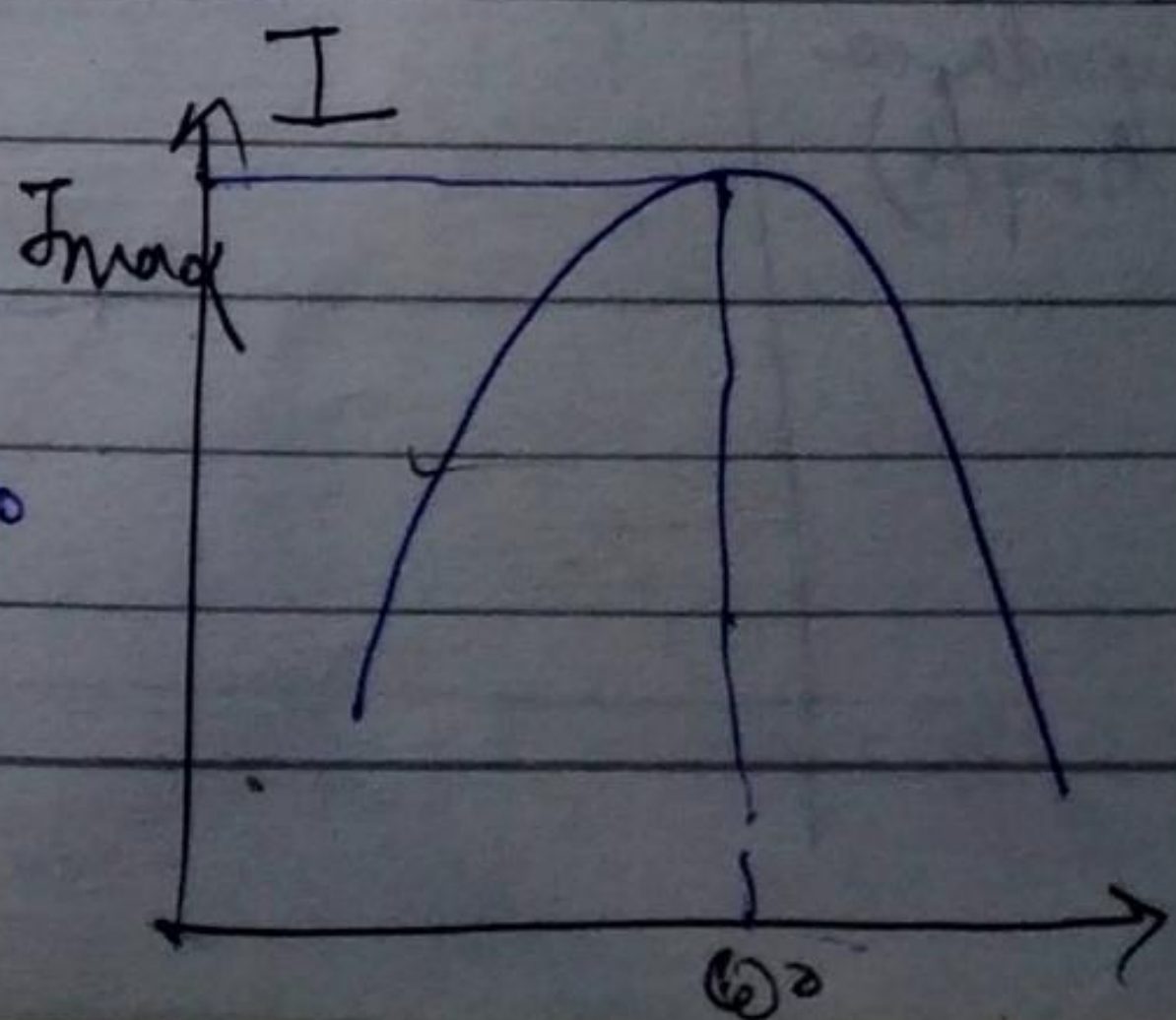means at  $\omega_0$   
at  $Z_{min}$  current  
will be  
max





From the graphs we can conclude the following points—

→ for  $\omega < \omega_0$  the capacitive Reactance  $>$  Inductive Reactance  $[X_C > X_L]$  and therefore the net reactance capacitive in nature. And hence the current  $\bar{I}$  leads the applied voltage  $\bar{V}$  and gives the leading pf.

→ At  $\omega = \omega_0$  both the reactances are equal and hence the impedance is min i.e.  $\underline{Z} = R$ , the current  $\bar{I}$  and  $\bar{V}$  are in phase and hence the pf is unity.

→ At  $\omega > \omega_0$  the inductive Reactance  $>$  capacitive Reactance  $[X_L > X_C]$  and  $\therefore$  the net reactance is inductive in nature and the current  $\bar{I}$  lags the applied voltage  $\bar{V}$ . Giving lagging pf.

→ At Resonance Net Reactive voltage = 0



$$I = \frac{V}{R + j(X_L - X_C)}$$

$$|I| = \frac{V}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

Voltage across capacitor -

$$V_C = I \cdot X_C$$

$$V_C = \frac{V}{\omega C \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} \Rightarrow \frac{dV_C}{d\omega} = 0$$

$$f_C = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - \frac{R^2 C}{2L}}$$

→ The frequency at which  $V_C$  is max.

Voltage across inductor -

$$V_L = I \cdot X_L = \frac{V}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

$$\frac{dV_L}{d\omega} = 0$$

$$f_L = \frac{1}{2\pi\sqrt{LC}} \sqrt{\left(\frac{L - R^2 C}{2L}\right)}$$

→ The frequency at which  $V_L$  is max.

Quality Factor :

→ Q.F. is a Ratio of the max energy stored in the ckt to the energy dissipated in the ckt in one time period.



$$Q = 2\pi \times \frac{\text{Max energy stored in the CKT}}{\text{(Energy dissipated per cycle of oscillation)}}$$

$$i(t) = I_m \sin \omega t$$

$$W_g = \frac{1}{2} L i^2 + \frac{1}{2} C V_c^2$$

$$V_c = \frac{1}{C} \int i dt$$

$$V_c = \frac{1}{C} \int I_m \sin \omega t dt = -\frac{I_m}{\omega C} \cos \omega t$$

$$W_g = \frac{1}{2} L [I_m \sin \omega t]^2 + \frac{1}{2} C \left[ -\frac{I_m}{\omega C} \cos \omega t \right]^2$$

$$W_g = \frac{1}{2} L I_m^2 \sin^2 \omega t + \frac{1}{2} \cancel{C} \frac{I_m^2}{\omega^2 \cancel{C}} \cos^2 \omega t$$

$$\omega = \frac{1}{\sqrt{LC}} \rightarrow \omega^2 = \frac{1}{LC} \Rightarrow L = \frac{1}{\omega^2 C}$$

$$W_g = \frac{1}{2} L I_m^2 \sin^2 \omega t + \frac{1}{2} L I_m^2 \cos^2 \omega t$$

$$W_g = \frac{1}{2} L I_m^2 [\sin^2 \omega t + \cos^2 \omega t]$$

$$\boxed{W_g = \frac{1}{2} L I_m^2}$$

$$Q = 2\pi \frac{\frac{1}{2} L I_m^2}{\left( \frac{I_m}{I_r} \right)^2 R \cdot \frac{1}{f}} \Rightarrow$$

$$\boxed{Q = \frac{\omega L}{R}}$$

$$Q = \frac{1}{\sqrt{LC}} \cdot \frac{L}{R}$$

$$\boxed{Q = \frac{1}{R} \sqrt{\frac{L}{C}}}$$



$$Q = \frac{\omega L}{R} = \frac{X_L}{R}$$

$$Q = \frac{I X_L}{I R} = \frac{V_L}{V_R} = \frac{V_C}{V_R} \quad \left( \text{At Resonance } V_L = V_C \right)$$

$$Q = \frac{I X_C}{I R} = \frac{X_C}{R} = \frac{1}{\omega R C}$$

$$Q = \frac{\omega L}{R} = \frac{1}{\omega R C}$$

$$Q = \frac{\text{Reactive Component of the voltage}}{\text{Active}}$$

$$Q = \frac{I^2 X_L}{I^2 R} = \frac{Q_L}{P}$$

At  $\omega = \omega_0$

$$1) V_R = I_R \cdot R = I R = \frac{V}{R} \cdot R \Rightarrow V \quad \boxed{V_R = V}$$

$$2) V_L = j X_L I_L = j X_L I = j \omega L \frac{V}{R} = j \left( \frac{\omega L}{R} \right) V$$

both are 180° out of phase  $V_L = +jQ V$   
so when we add

$$V = V_L + V_R + V_C$$

$$\boxed{V = V_R}$$

Amplification factor

$$3) V_C = -j X_C I_C = -j X_C I$$



$$= -j X_C \frac{V}{R} = -j \left( \frac{1}{\omega R C} \right) V$$

$$V_C = -jQ V$$



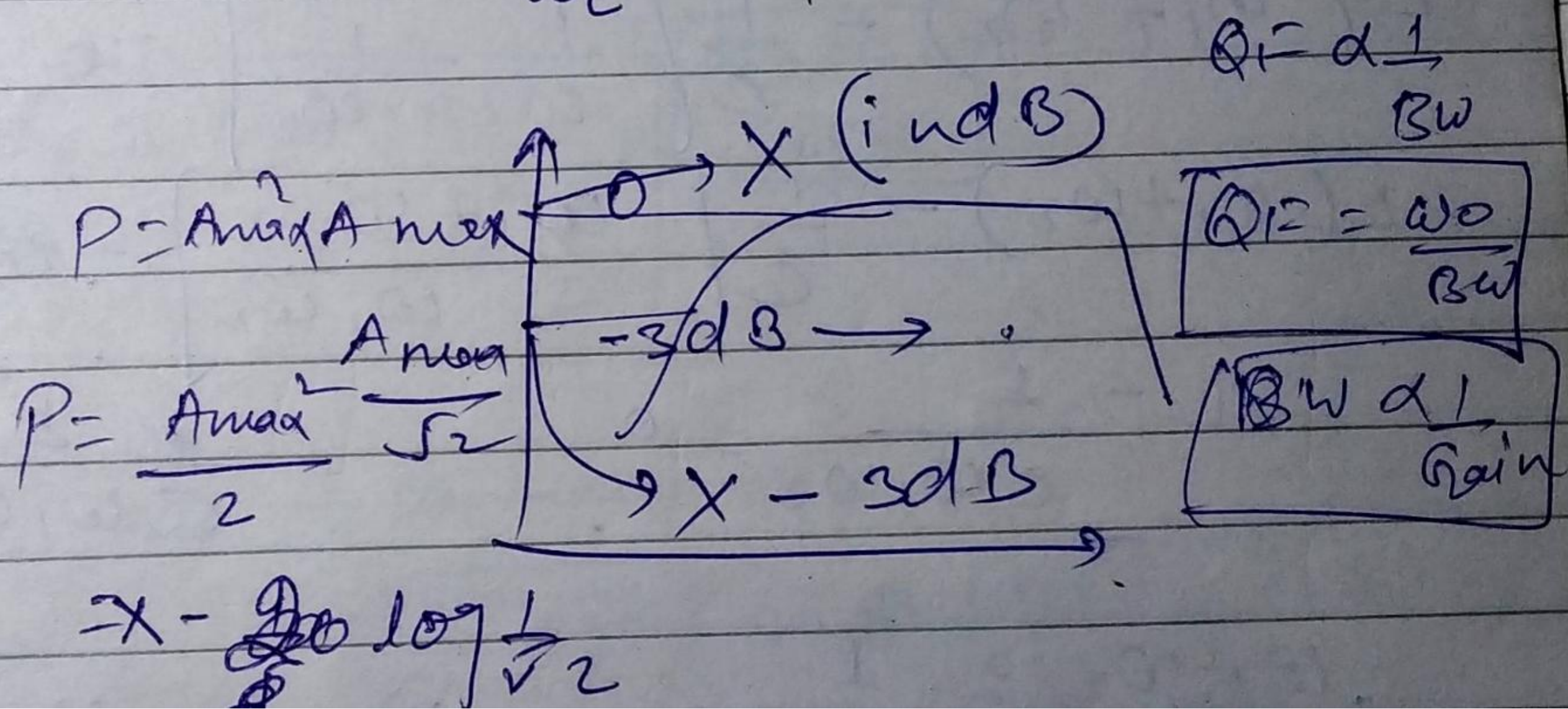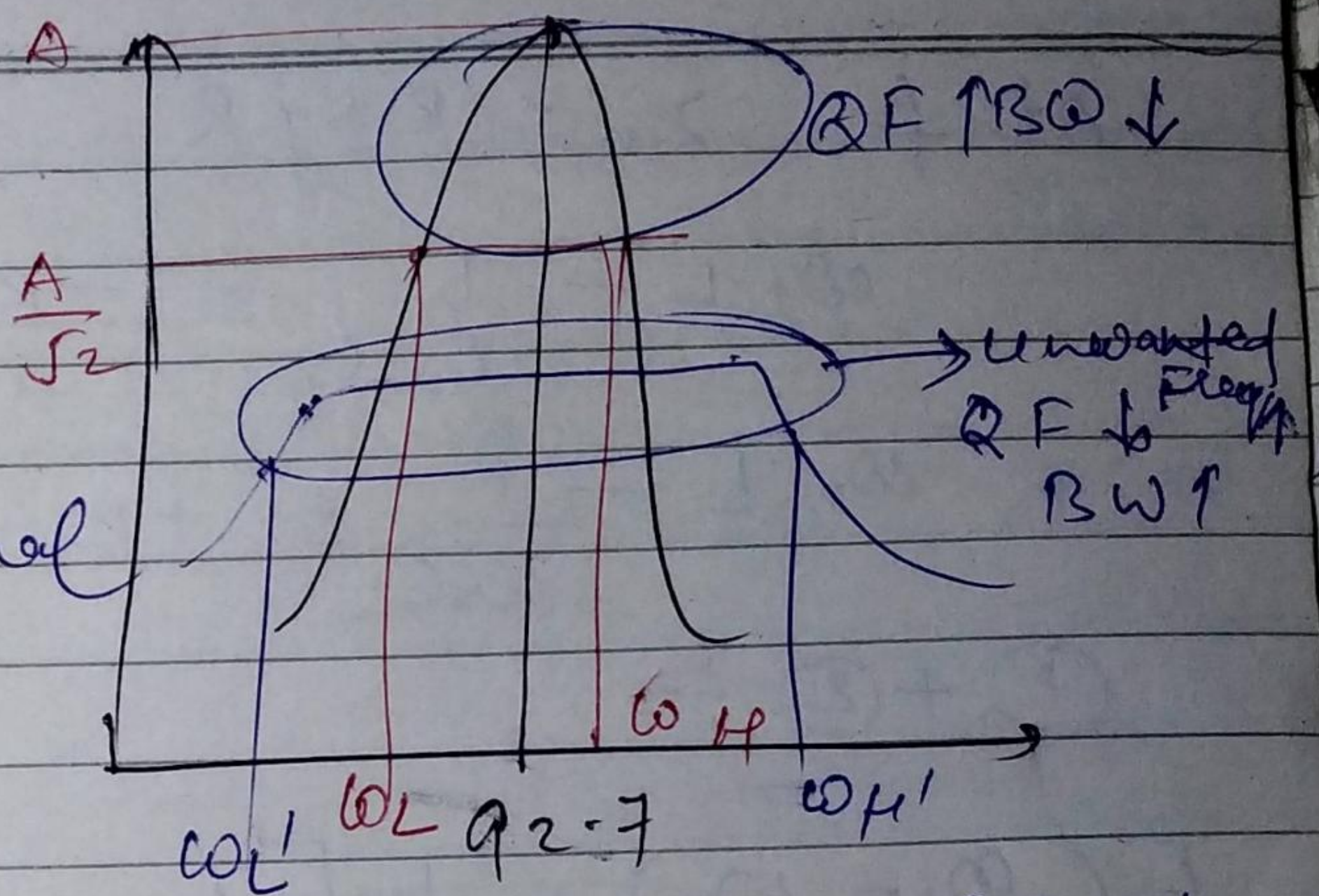
## Bandwidth:-

BW represents the range of frequencies for which power level in the signal is at least half of the max. power





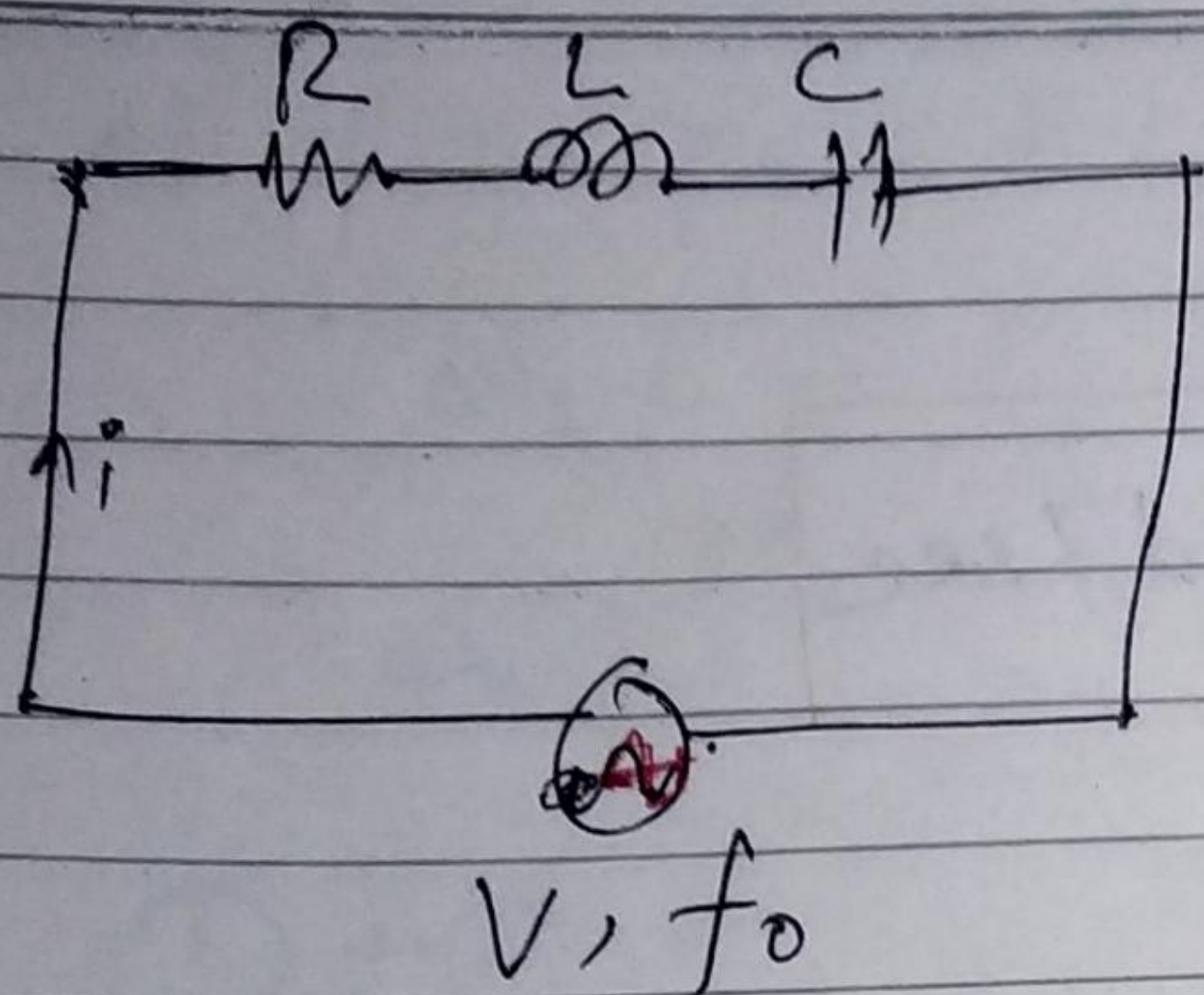

$$v = iR + L \frac{di}{dt} + \frac{1}{C} \int i dt$$

$$\frac{dv}{dt} = R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{i}{C}$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = \frac{1}{L} \frac{dv}{dt}$$

characteristic eqn —

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$\swarrow \beta \omega$ 
 $\swarrow \omega^2$

$$s^2 + 2\zeta \omega_n s + \omega_n^2 = 0$$

$$2\zeta \omega_n = \frac{R}{L}$$

$$\zeta = \frac{R}{2L} \cdot \frac{1}{\omega_n} = \frac{R}{2L} \cdot \frac{\sqrt{LC}}{1}$$

$$\zeta = \frac{R}{2} \sqrt{\frac{C}{L}}$$


$$\zeta = \frac{1}{2Q}$$

System's Natural frequency = Resonant Frequency

$$\omega_n = \frac{1}{\sqrt{LC}}$$



## Parallel Resonance :-

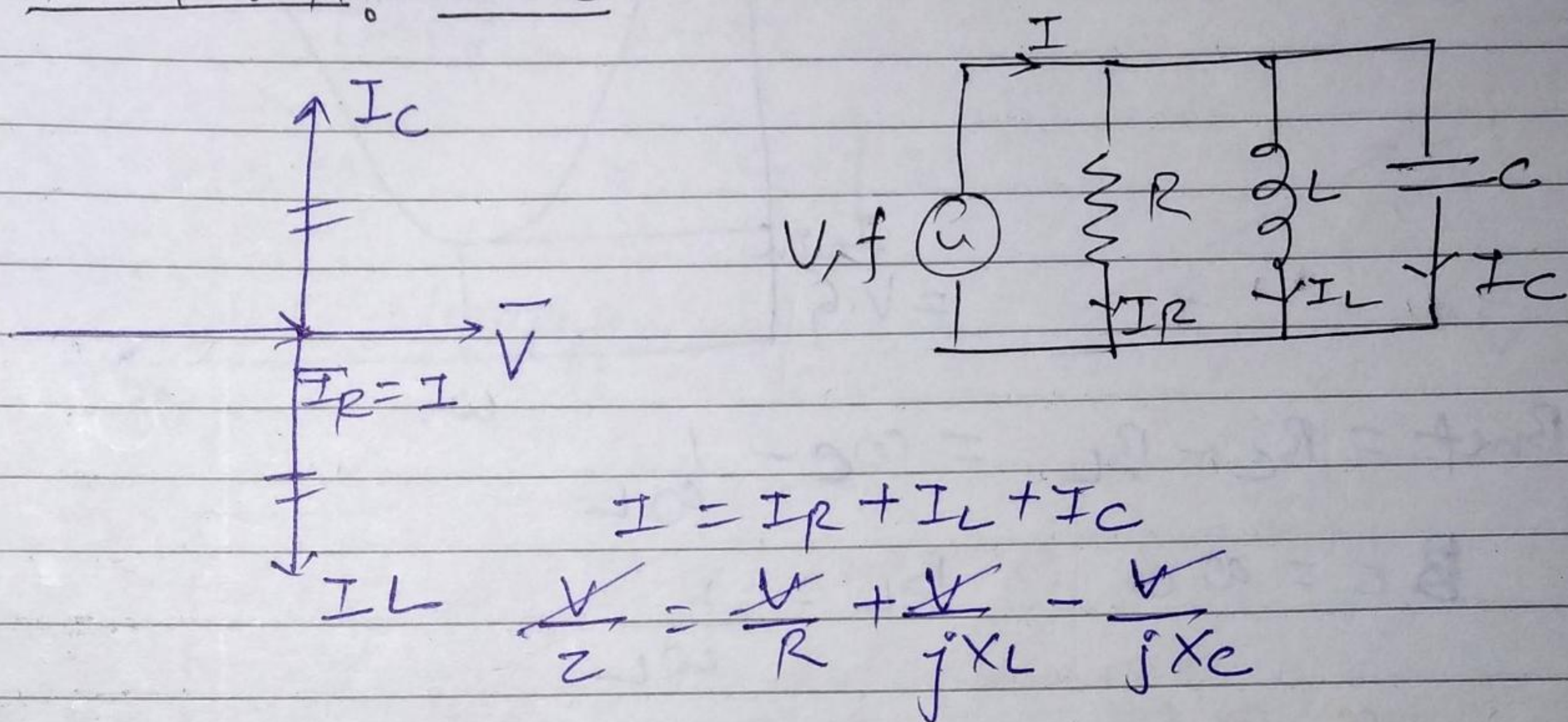

$$Y = G + j(B_C - B_L)$$

for Resonant  $B_C = B_L$


$$\omega_0 C = \frac{1}{\omega_0 L}$$

$$\omega_0^2 = \frac{1}{LC}$$

$$\boxed{\omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/sec}}$$


$$\textcircled{1} Y = G + j(B_C - B_L)$$

$$Y = G + j\left(\omega C - \frac{1}{\omega L}\right) \quad |Y| = \sqrt{G^2 + \left(\omega C - \frac{1}{\omega L}\right)^2}$$

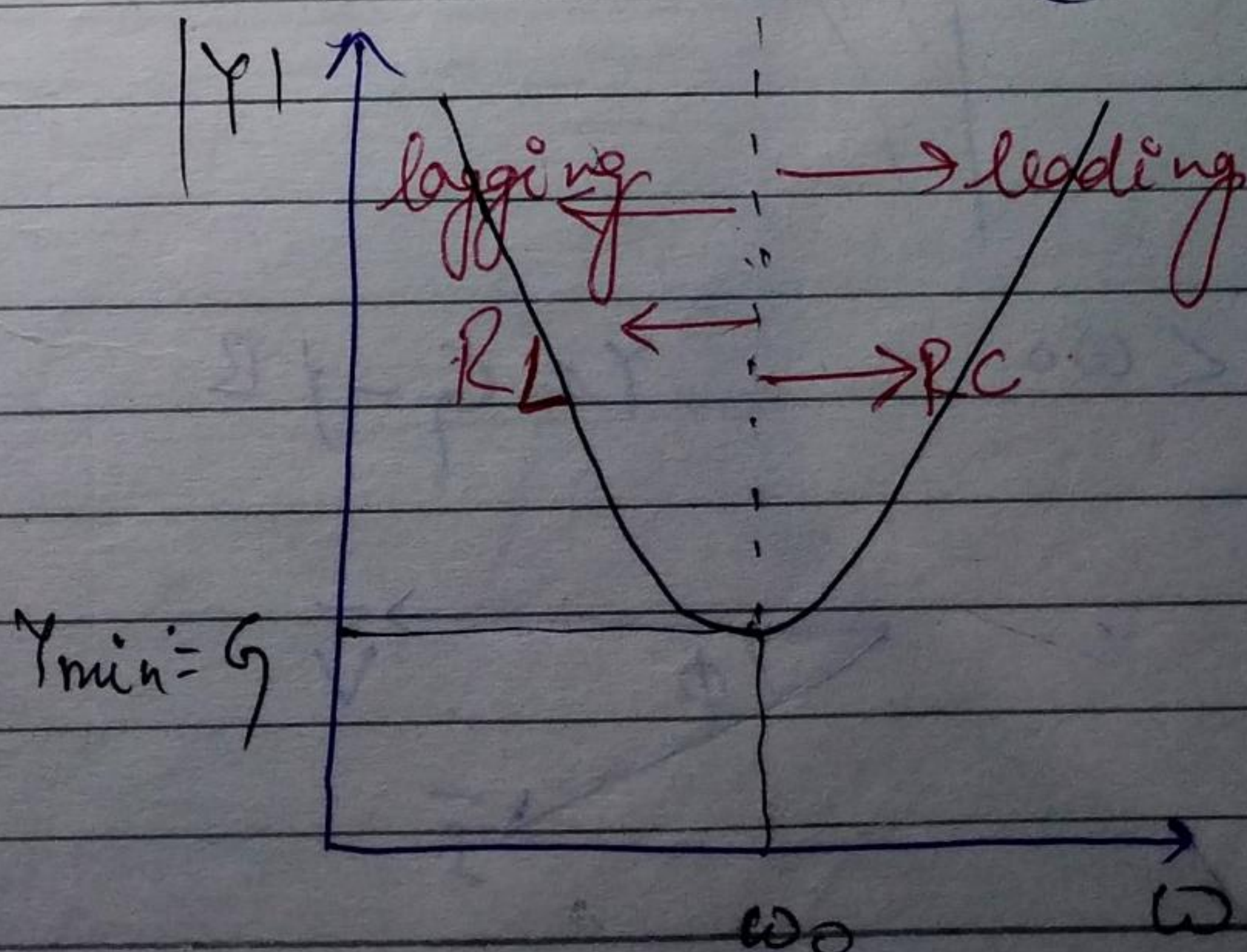



②  $I = \frac{V}{|Z|}$        $I = V/Y$

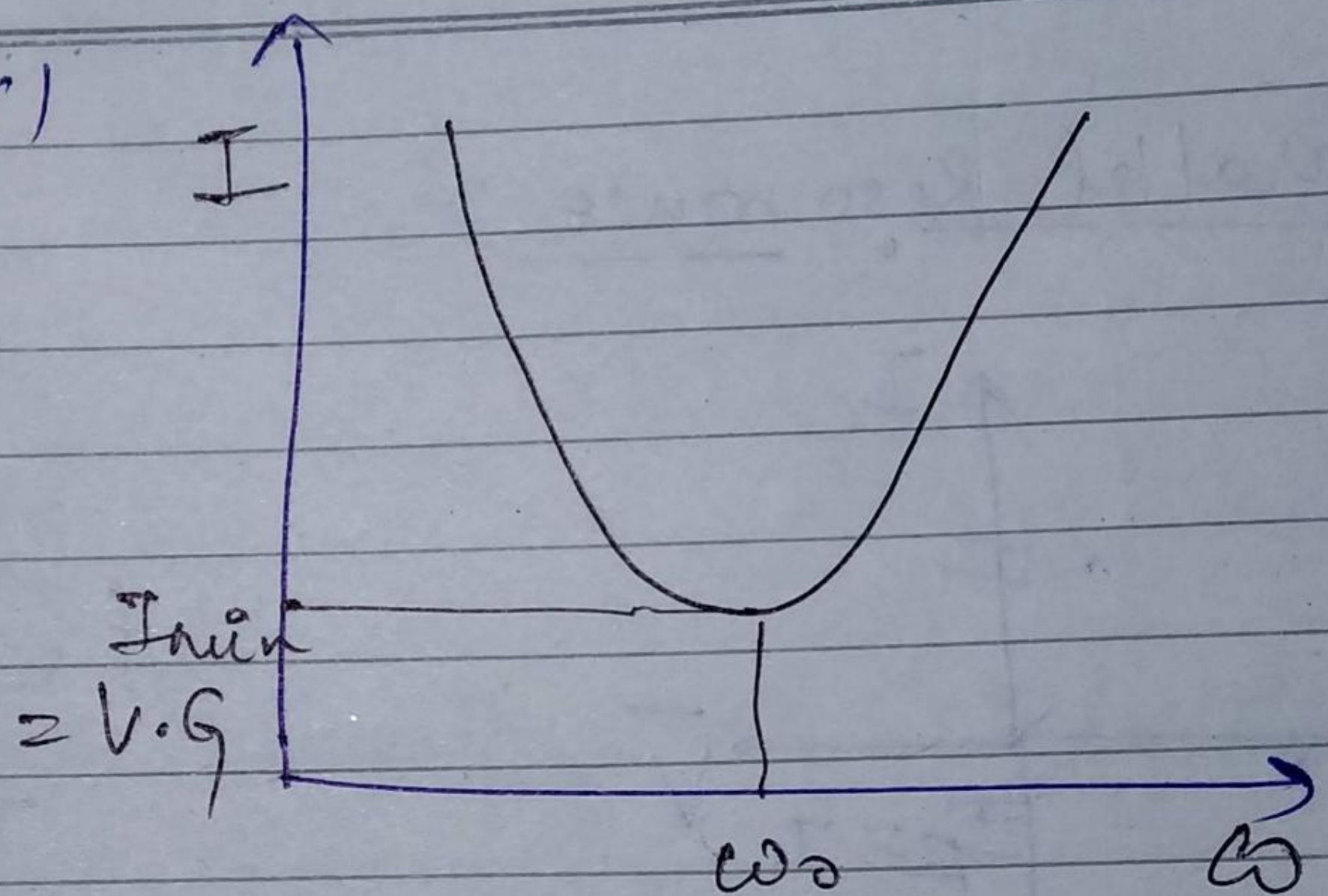



Quality factor -

$$Q = \frac{\text{Reactive Component of Current}}{\text{Active}}$$

$$Q = \frac{I_L \text{ or } I_C}{IR} = \frac{\frac{V}{X_L} \text{ or } \frac{V}{X_C}}{V/R}$$

$$Q = \frac{R}{X_L} \text{ or } \frac{R}{X_C}$$


$$\begin{aligned} Q &= \frac{R}{\omega L} \\ Q &= \omega R C \end{aligned}$$



$$Q = \frac{R}{L} \cdot \sqrt{\frac{LC}{I}} \Rightarrow \boxed{Q = R \sqrt{\frac{C}{L}}}$$



Ques:- In the given ckt find

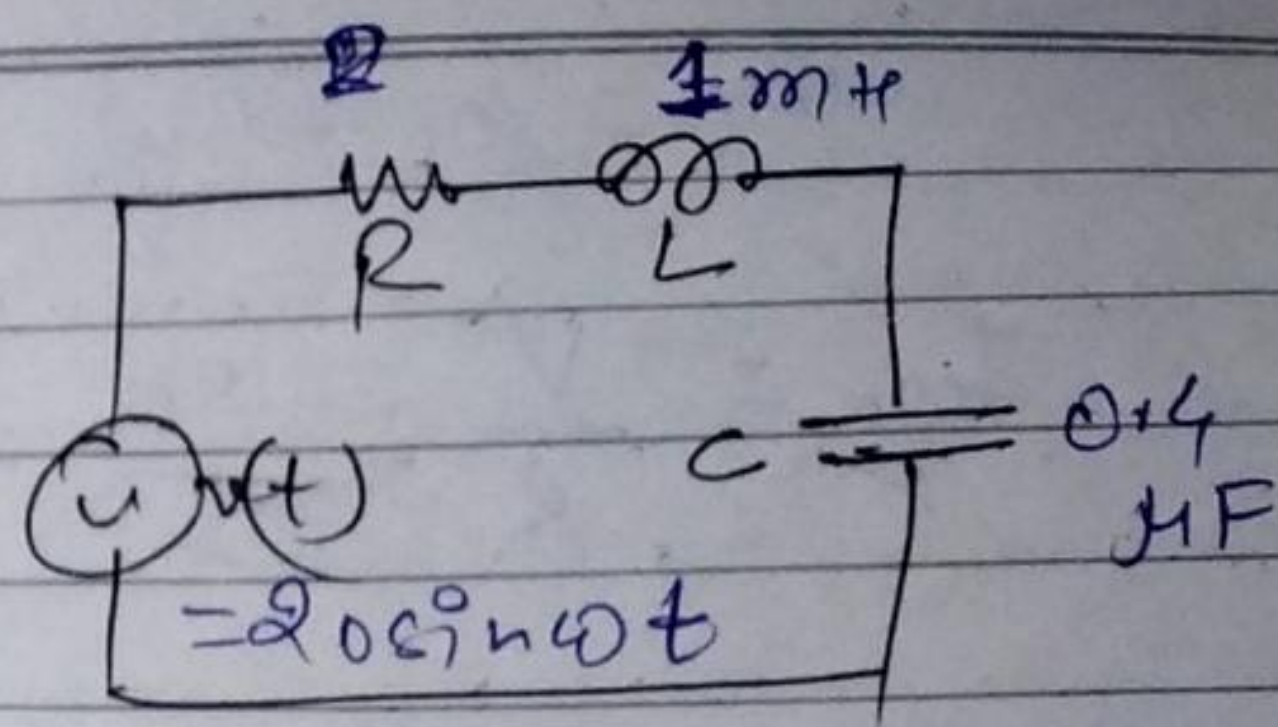

(a) Resonant Frequency at the half power frequencies.

(b) Q f and B.W.

(c) Amplitude of the current at resonant frequency and half power frequencies.

$$(a) \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-3} \times 0.4 \times 10^{-6}}}$$

$$\omega_0 = 50 \text{ K rad/sec.}$$

$$\text{At } \omega_1, \omega_2 \quad Z = \sqrt{2} R$$

$$\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} = \sqrt{2} R$$

$$\omega_1 = \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$BW = \frac{R}{L} \stackrel{\text{or}}{=} \frac{2}{1 \text{ mH}} = 2 \text{ K rad/sec}$$

$$Q = \frac{\omega_0}{BW} = \frac{50 \text{ K}}{2 \text{ K}} \quad \boxed{Q = 25}$$

$$\omega_1 = \omega_0 - \frac{BW}{2} = 49 \text{ K rad/sec}$$