
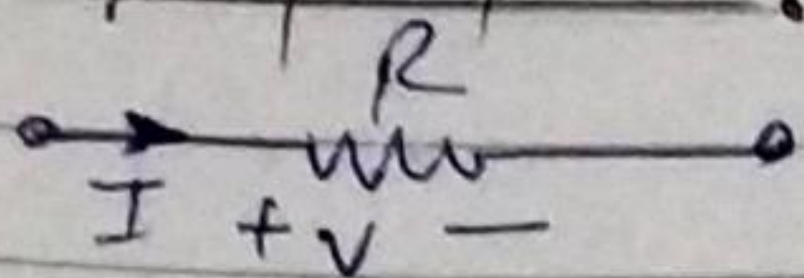


Theorems :-


Superposition Theorem :-



 $V = IR$

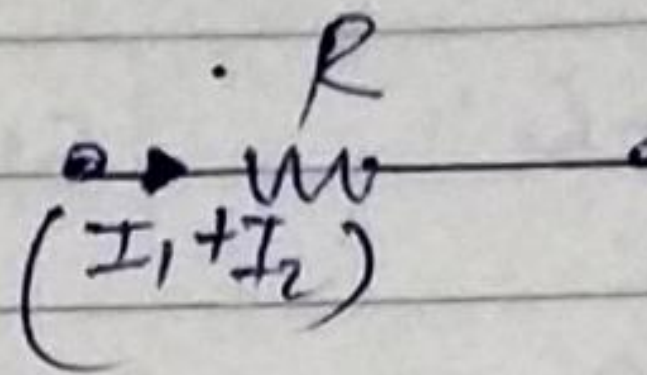


It follows law of additivity

$$\begin{aligned}
 V' &= (I_1 + I_2)R \\
 &= I_1 R + I_2 R \\
 &= V_1 + V_2
 \end{aligned}$$

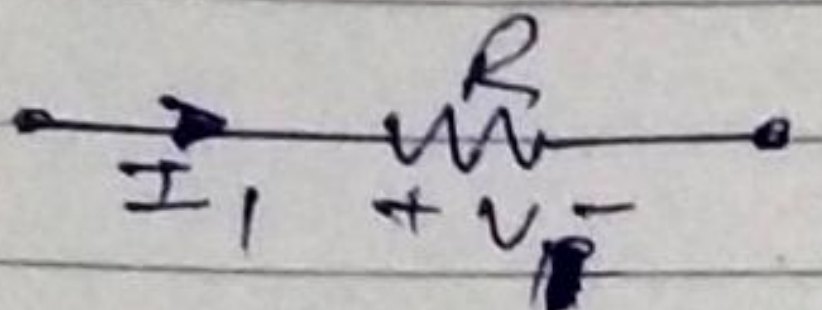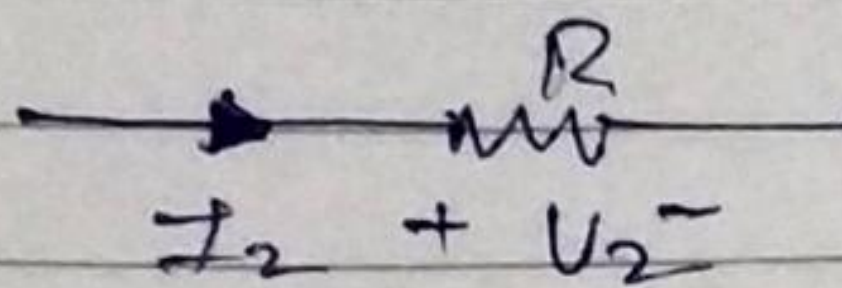

 $V_1 = I_1 R$


 $V_2 = I_2 R$

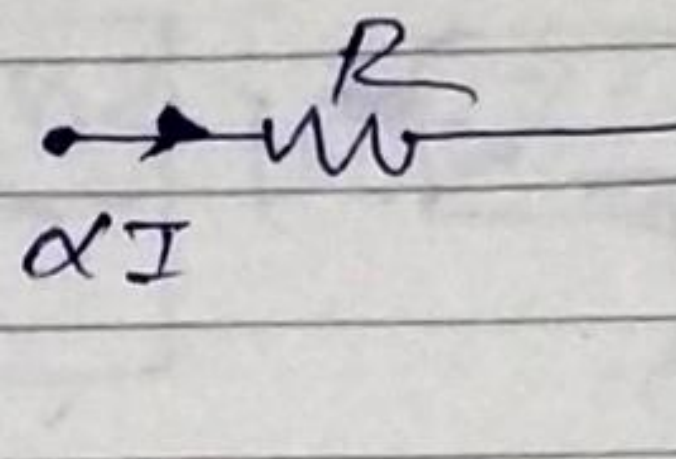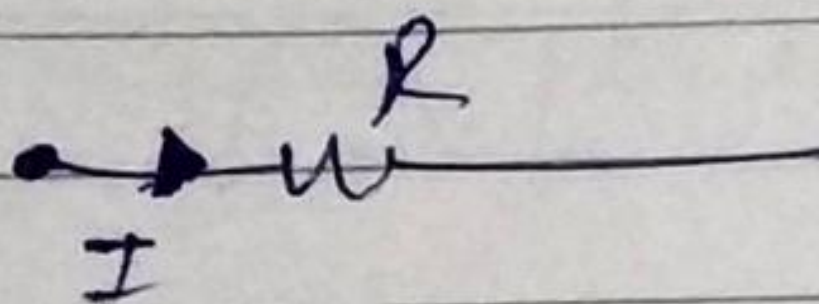

$$\begin{aligned}
 V'' &= (\alpha I) R \\
 &= \alpha (IR) \\
 &= \alpha V
 \end{aligned}$$

It follows law of homogeneity so it is linear.


 $P = I^2 R$


Non Linear due to NL operator. (square)

→ In a Linear Bilateral NID containing more than one independent voltage and current source, the response in any element is the sum of the responses obtained with one source acting at a time and other sources be deactivated.


→ Deactivation means all independent sources are replaced by their internal resistance i.e. voltage source is replaced by S.C. and current source by O.C.
(Dependent sources remain as it is.)

Ques:- Find the current flow in 3 ohm resistor by the use of superposition theorem.

Case 1: 12V

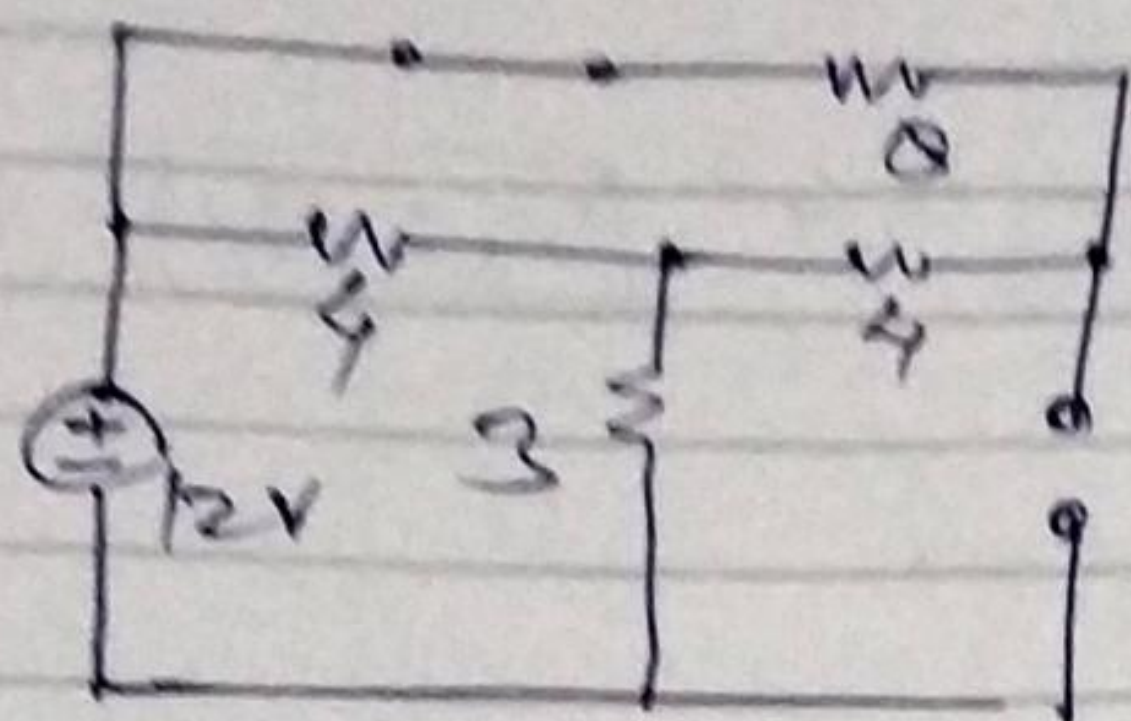


↓


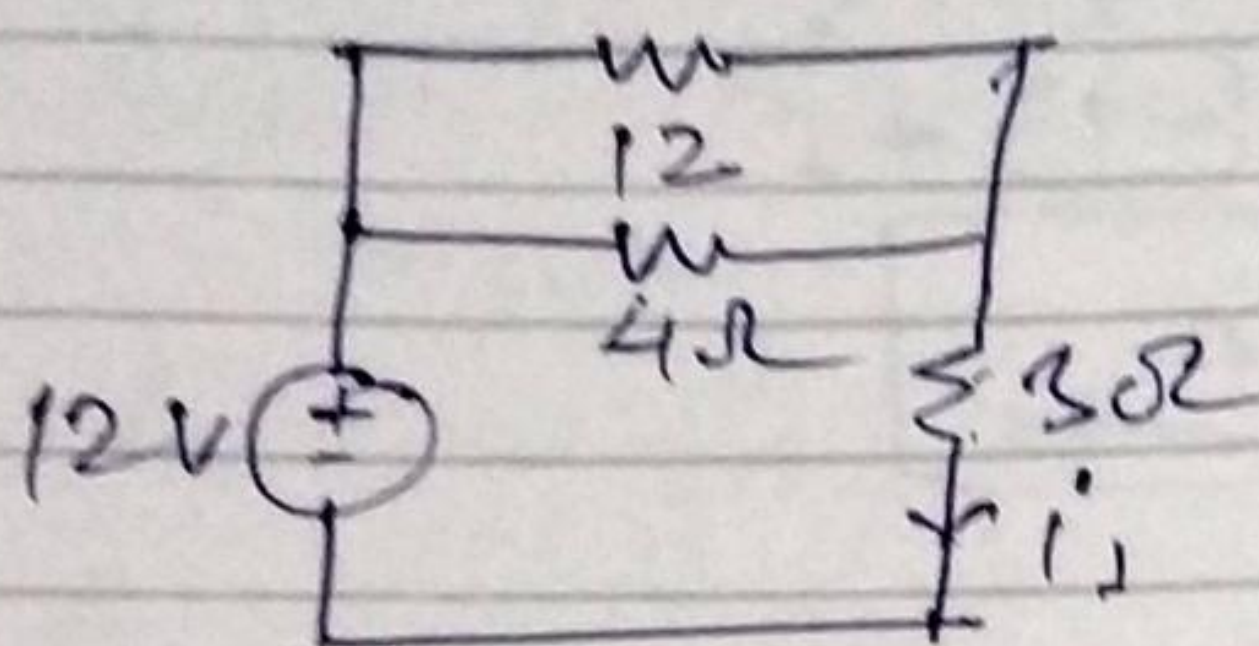


$$i_1 = \frac{12}{6}$$

$$i_1 = 2A$$

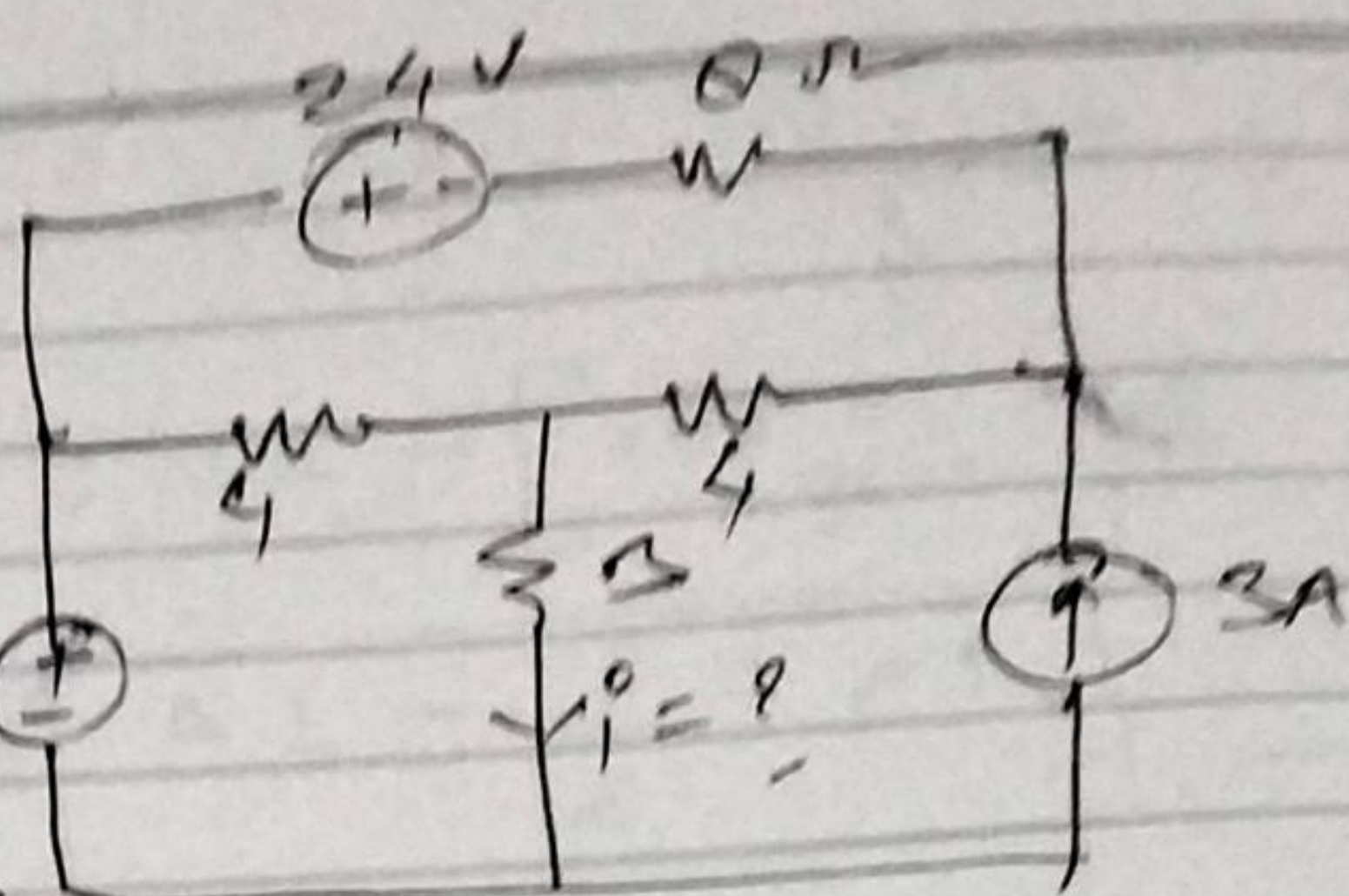

Case 2

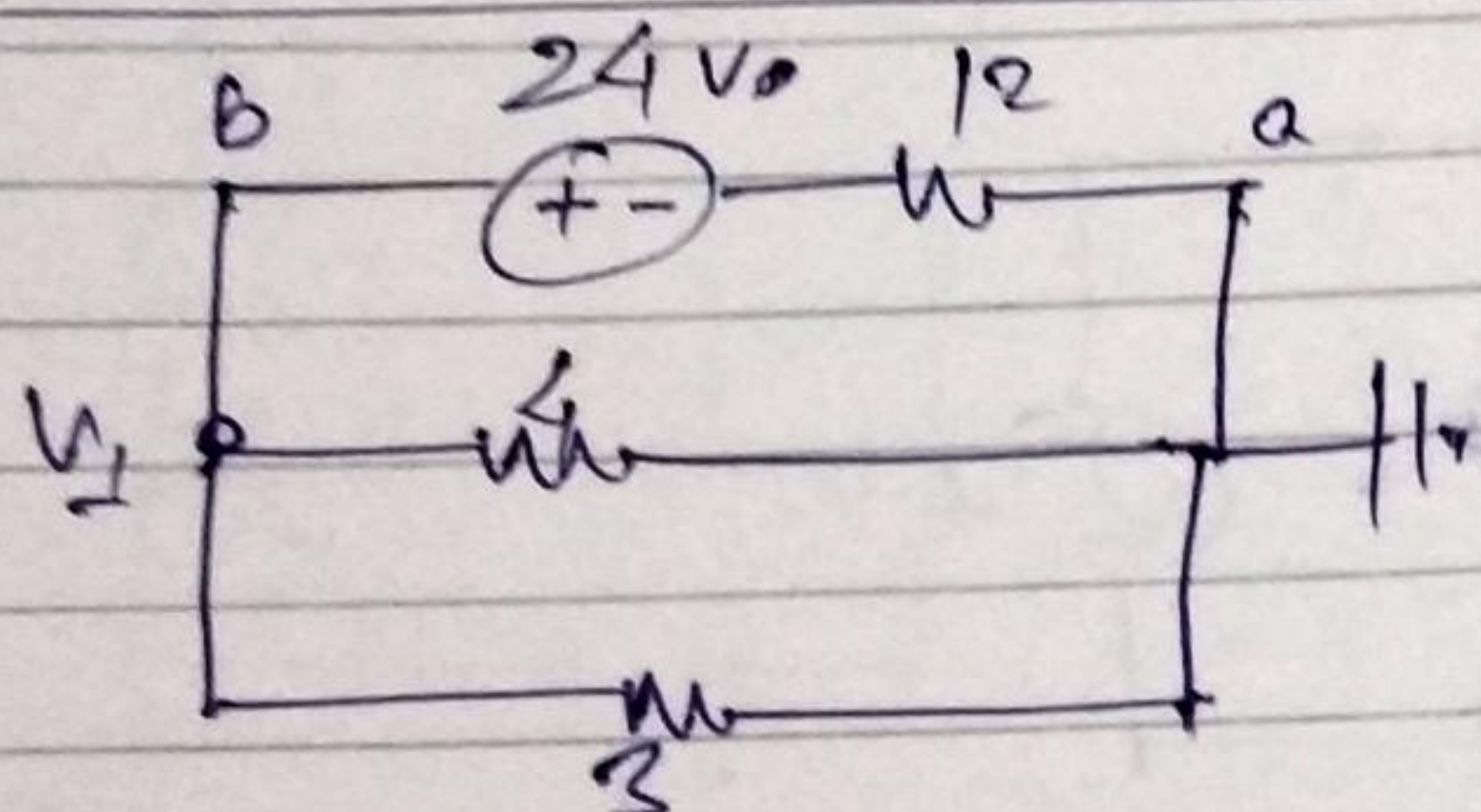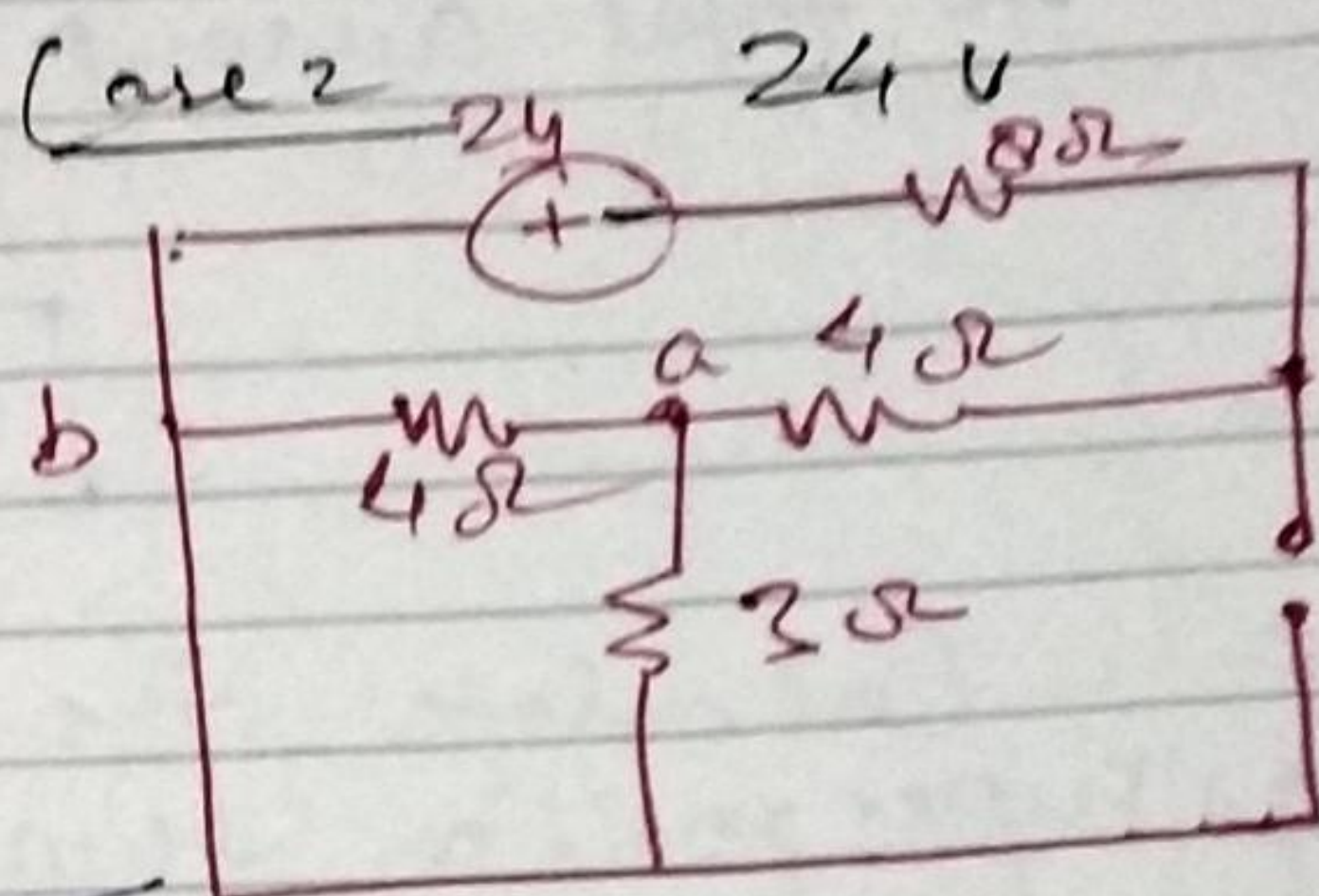

Apply Nodal


$$\frac{V_1 - 24}{12} + \frac{V_1}{4} + \frac{V_1}{3} = 0$$

$$V_1 - 24 + 3V_1 + 4V_1 = 0$$

$$V_1 = 3V$$

$$i_2 = \frac{0 - V_1}{3} = \frac{0 - 3}{3} \quad i_2 = -1A$$

Case 3:

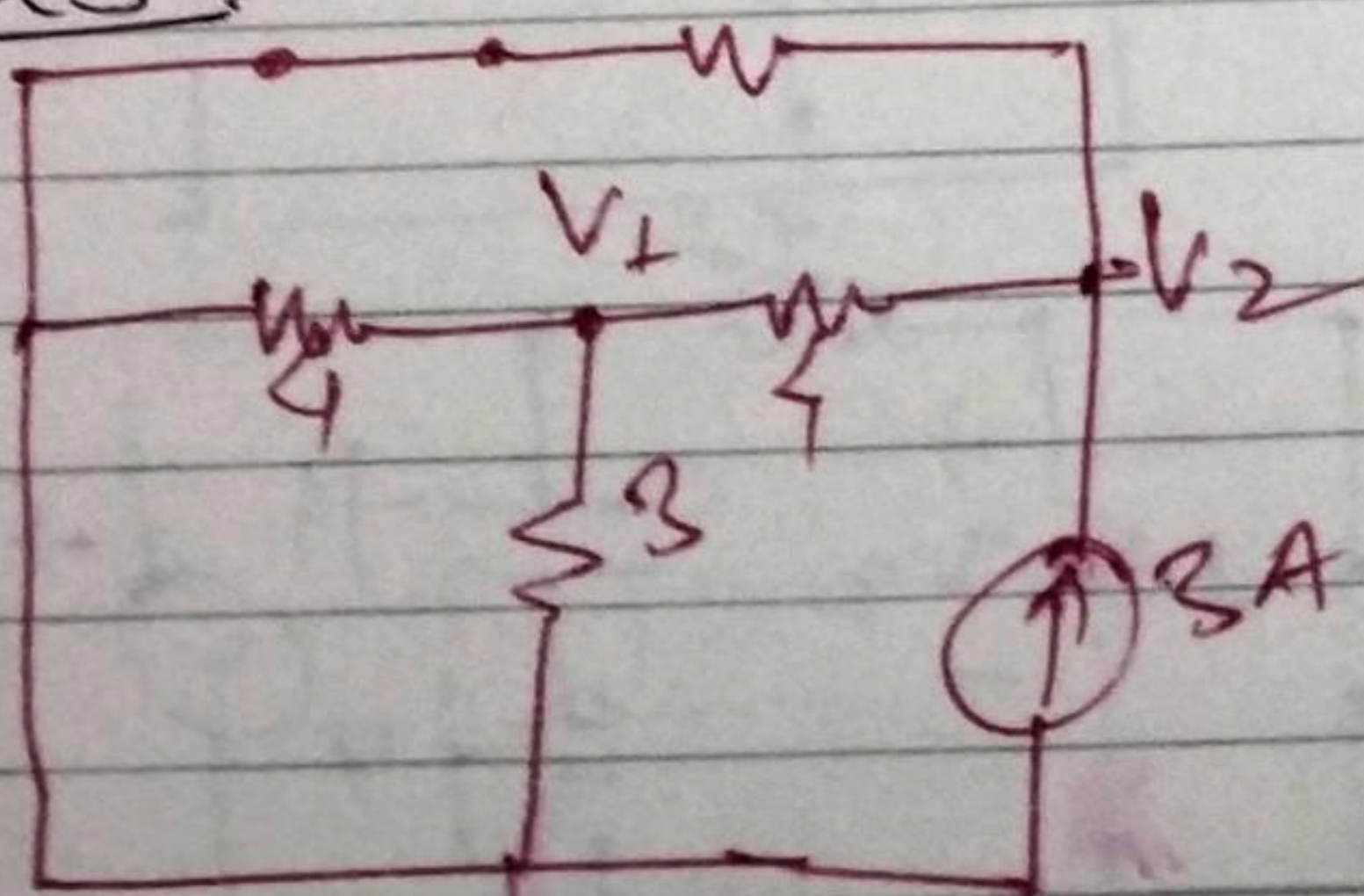

$$\frac{V_1}{4} + \frac{V_1}{3} + \frac{V_1 - V_2}{4} = 0$$

$$V_1 \left(\frac{10}{12} \right) = \frac{V_2}{4}$$

$$V_2 = \frac{10}{3} V_1$$

$$\frac{V_2}{8} + \frac{V_2 - V_1}{4} = 3$$

$$V_2 + 2V_2 - 2V_1 = 24$$

$$3 \left[\frac{10}{3} V_1 \right] - 2V_1 = 24$$

$$8V_1 = 24 \quad \boxed{V_1 = 3V}$$

$$\boxed{i_3 = \frac{3}{3} = 1A}$$


so total current

$$i = i_1 + i_2 + i_3$$


$$= 2 + (-1) + 1$$

$$\boxed{i = \underline{2A}}$$

Thevenin's Theorem:-

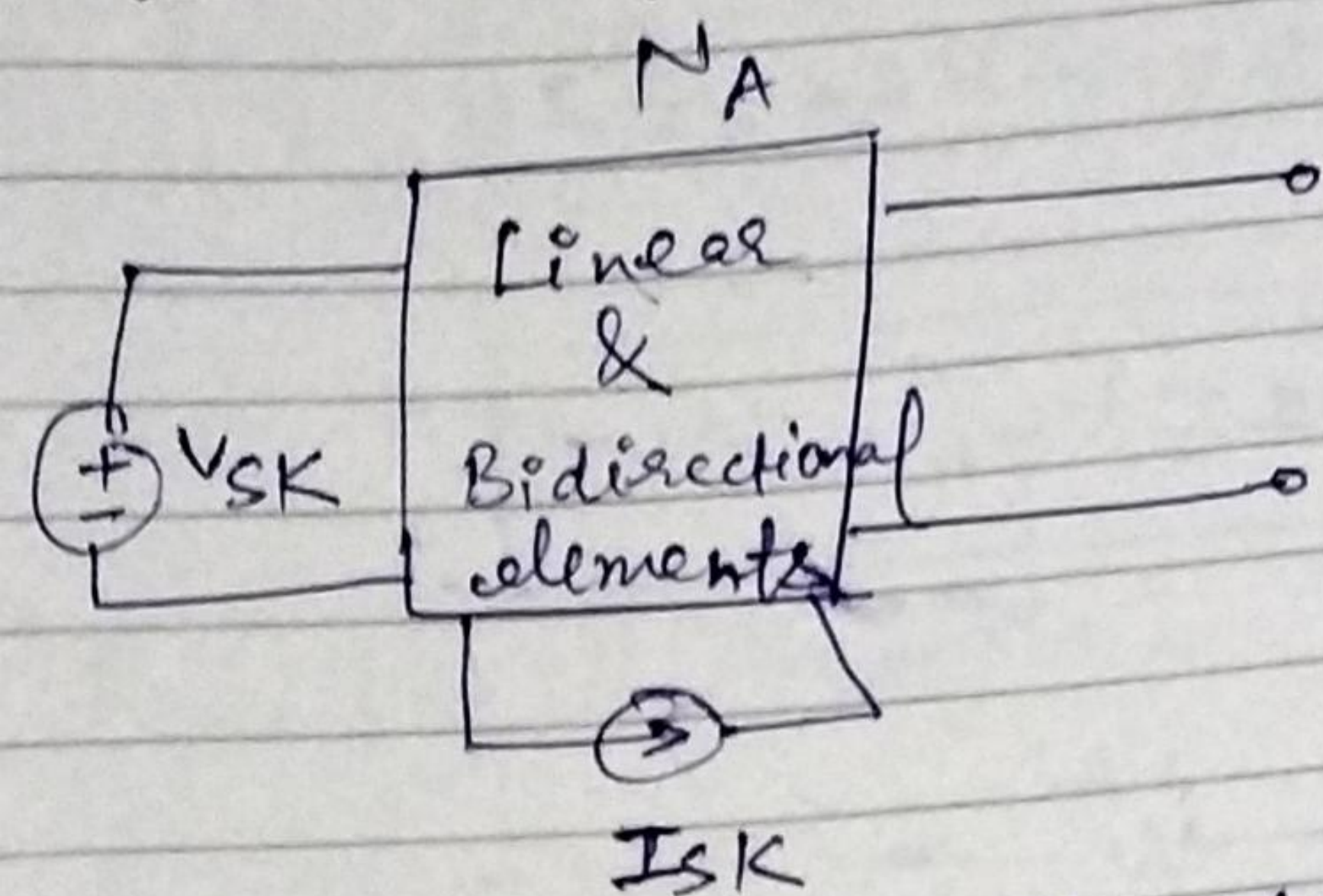


\Rightarrow

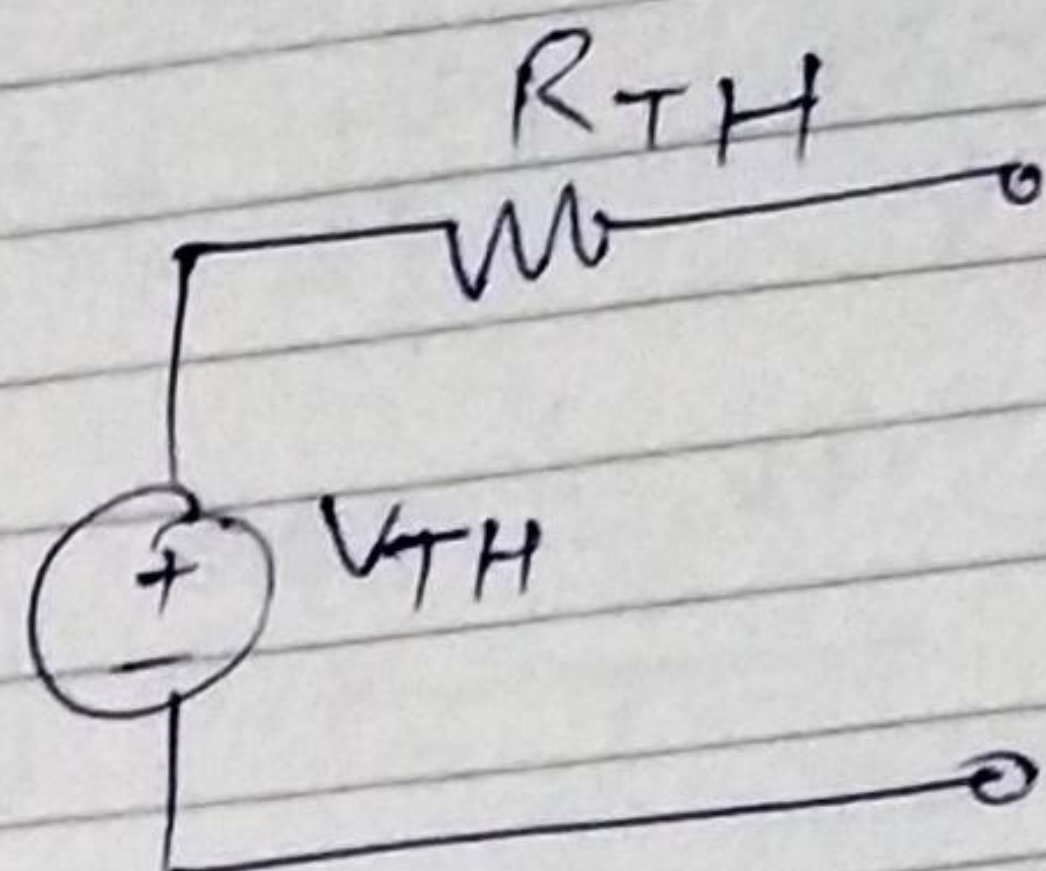


→ A Two terminal N/W ' N_A ' containing linear and bidirectional element and independent source is equivalent to a single N/W containing an equivalent voltage source ' V_{TH} ' in series with the resistance ' R_{TH} '.

→ The source voltage is the open CKT voltage across the terminals of the N/W (N_A) and resistance ' R_{TH} ' is the O/P resistance of ' N_A ' measured at its terminals after deactivating or independent sources in ' N_A '.

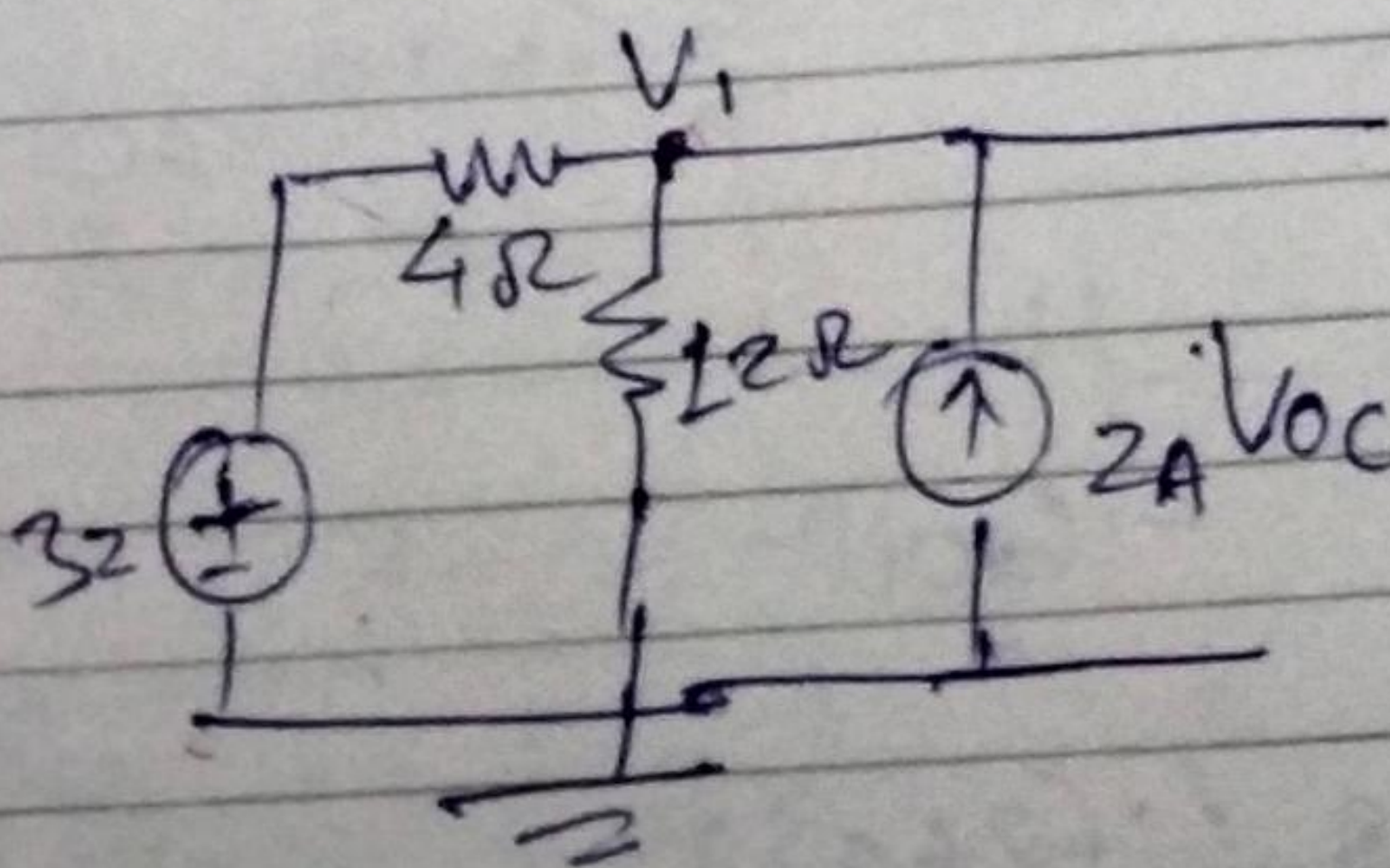Ques:- Find the current through (R_L) when ' R_L ' is 6Ω and 36Ω by using Thevenin's Theorem.



\leftarrow

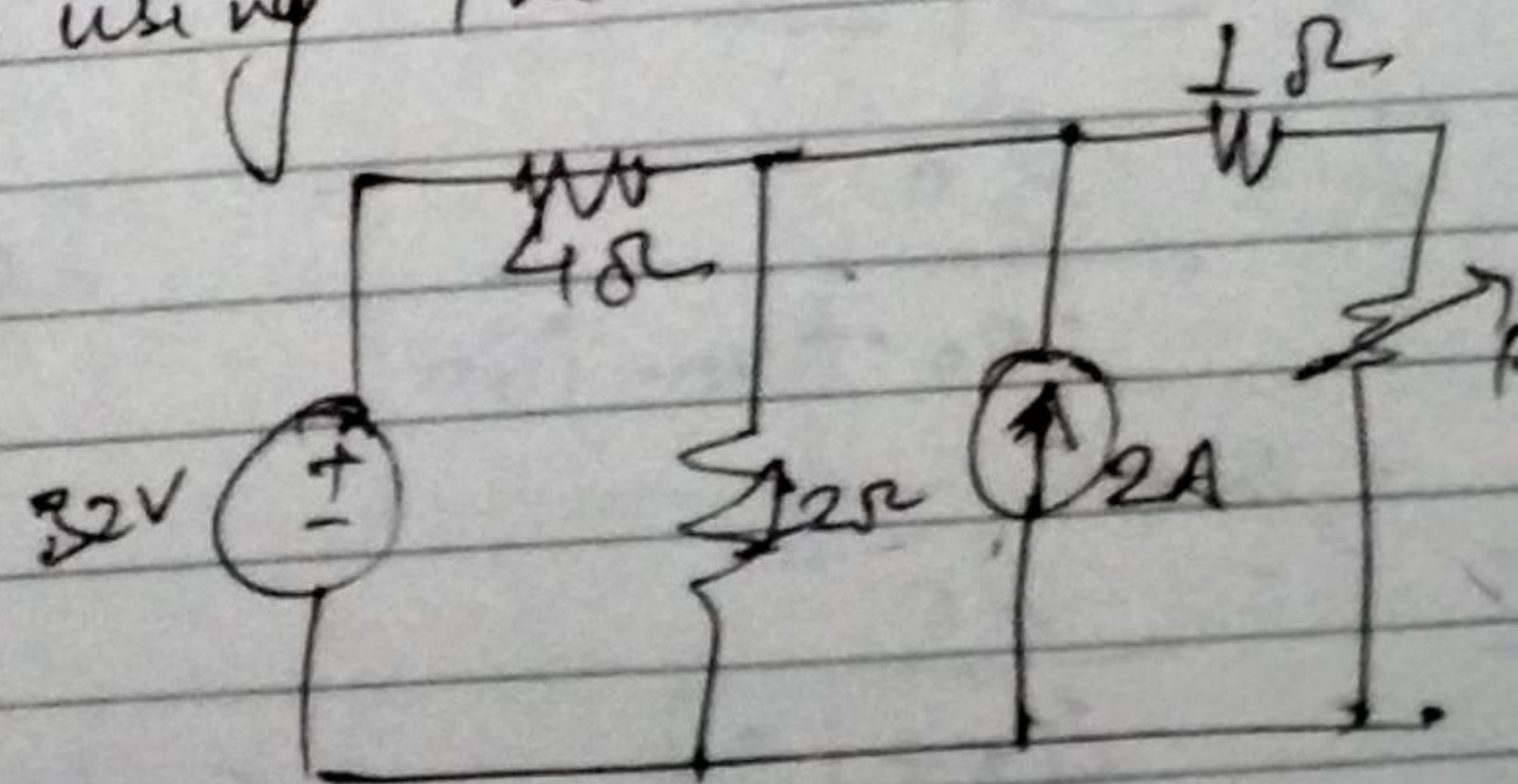

Case 1 V_{TH}


$$\frac{V_1 - 32}{4} + \frac{V_1}{12} - 2 = 0 \quad 3V_1 - 96 + V_1 = 24$$

$$4V_1 = 120 \quad \boxed{V_1 = V_{oc} = V_{TH} = 30V}$$

Case 2 R_{TH}

$$R_{TH} = (12 \parallel 4) + 1$$

$$\boxed{R_{TH} = 4\Omega}$$

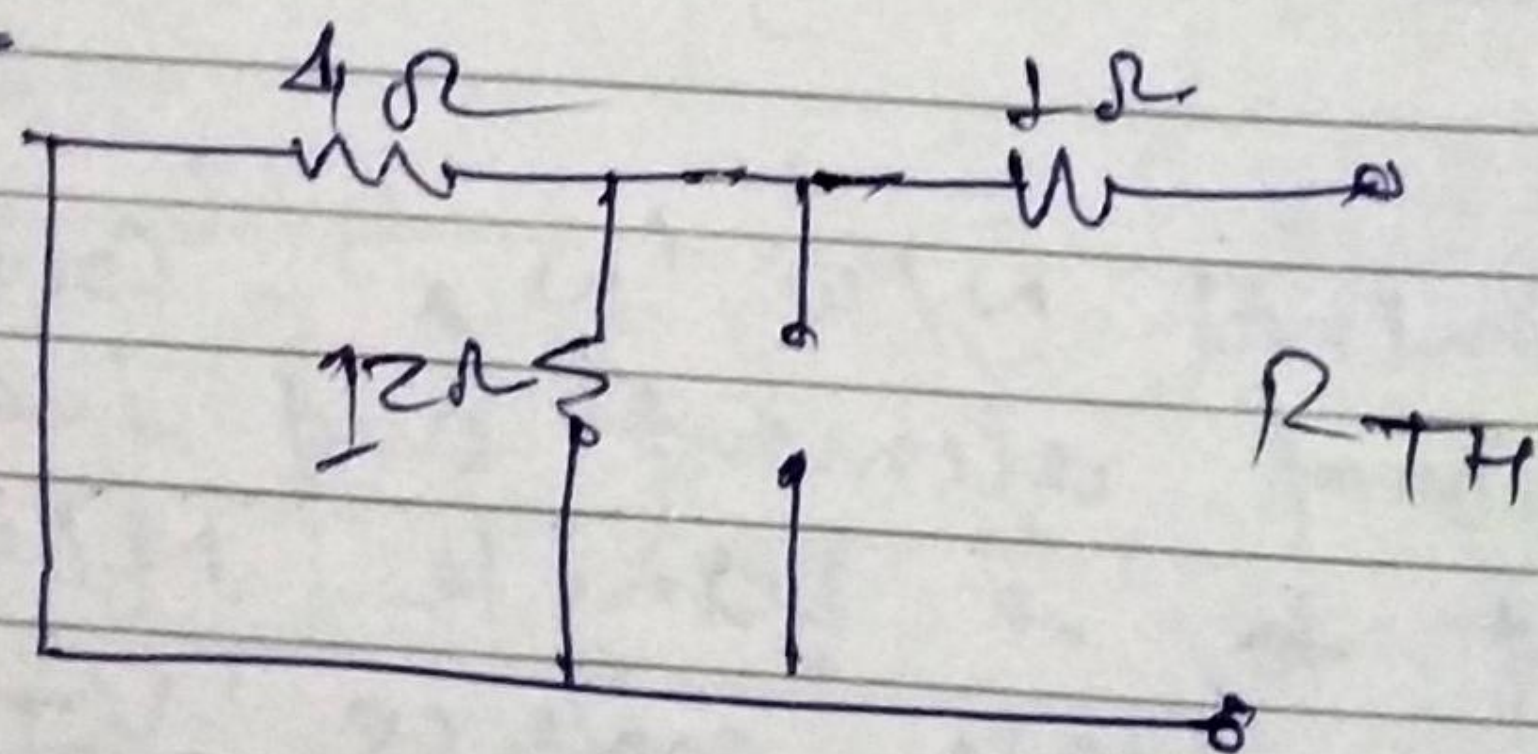


① $R_L = 6\Omega$

$$I = \frac{30}{4+6} = 3A$$


② $R_L = 36\Omega$

$$I = \frac{30}{40} = 0.75A$$

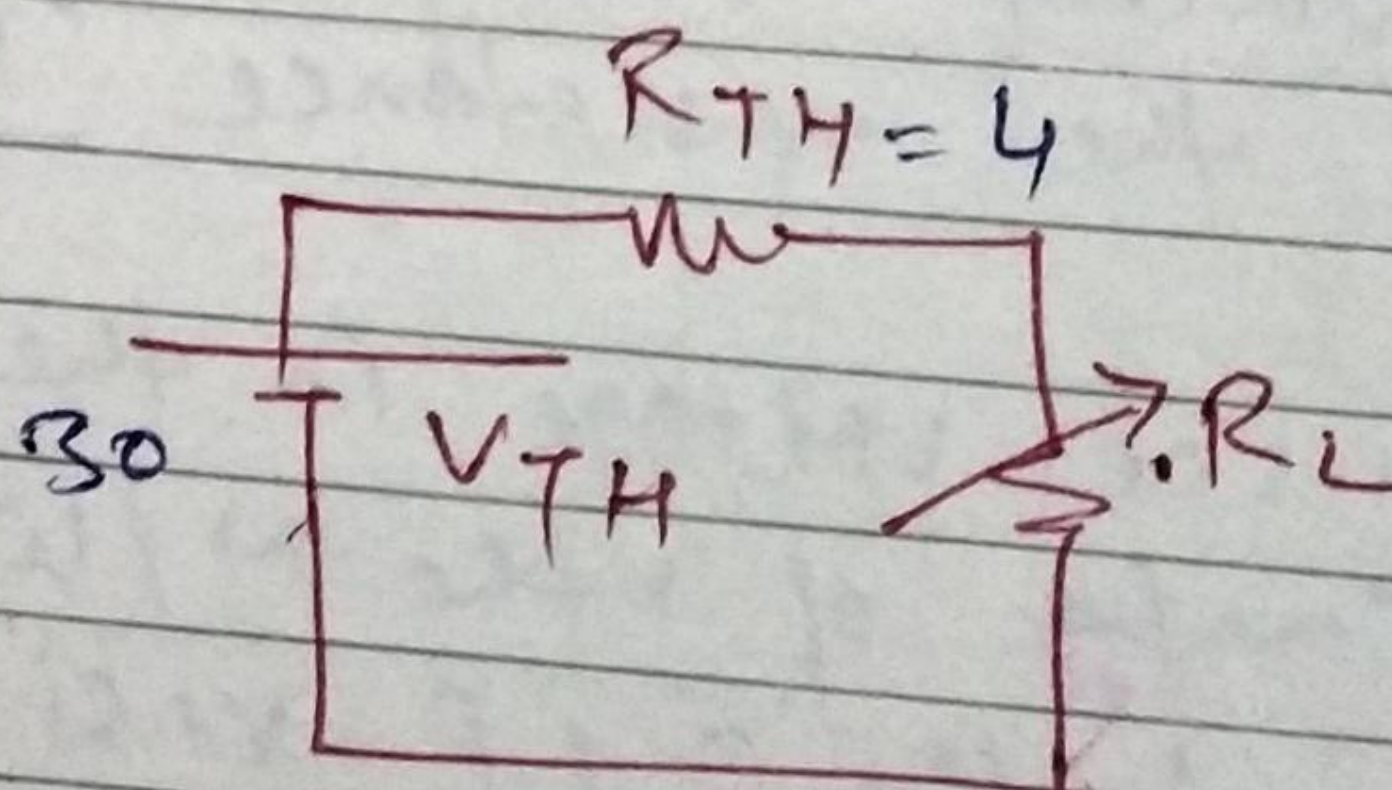

Ques :-

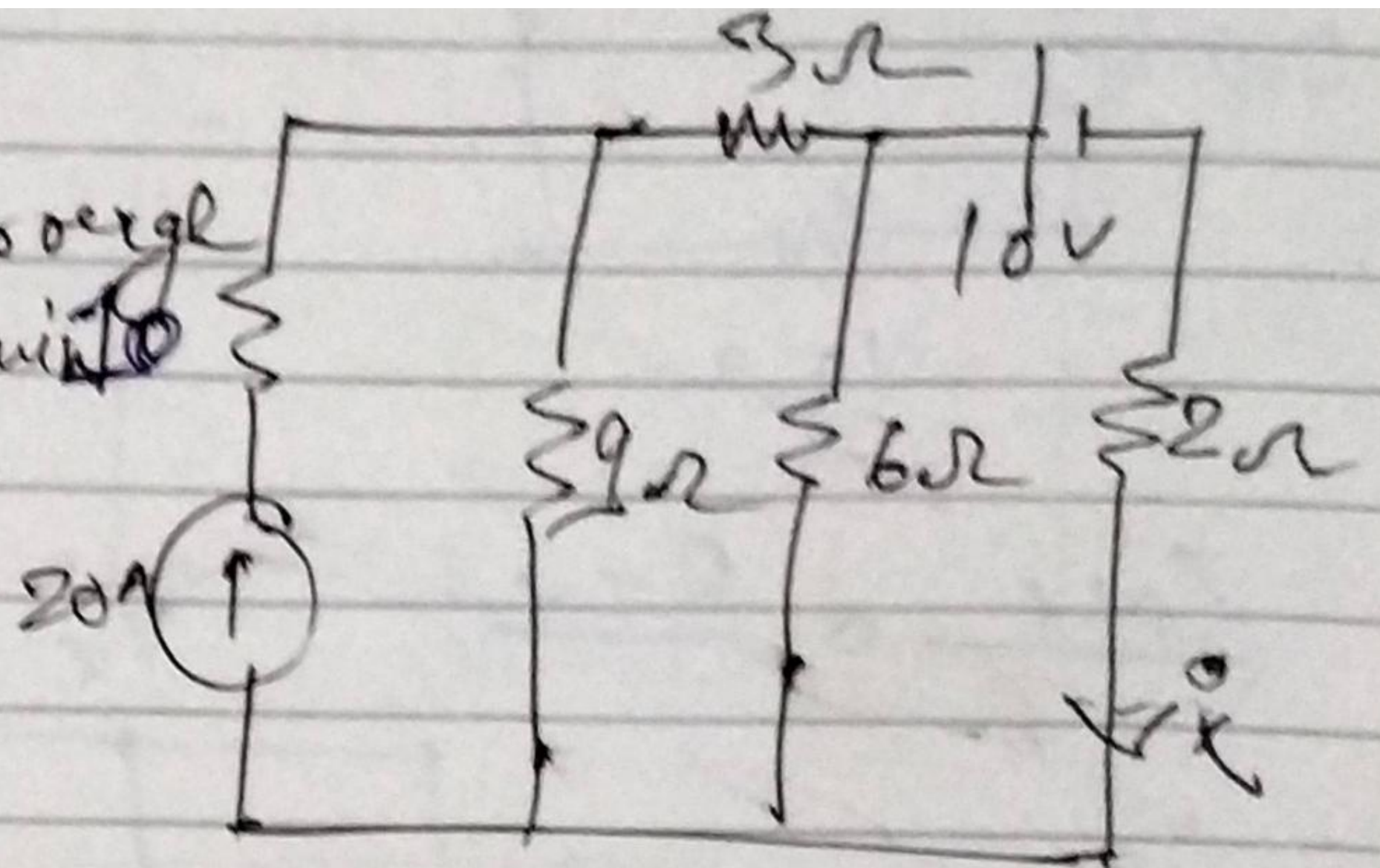Find current flowing through 2Ω resistor by using Thevenin's theorem.



Case :- V_{TH}



$$-V_{TH} - 10 + 60 = 0$$


$$V_{TH} = 50 \text{ Volts}$$

Case :- R_{TH}

$$(9 + 3) \parallel 6$$

$$R_{TH} = 4\Omega$$

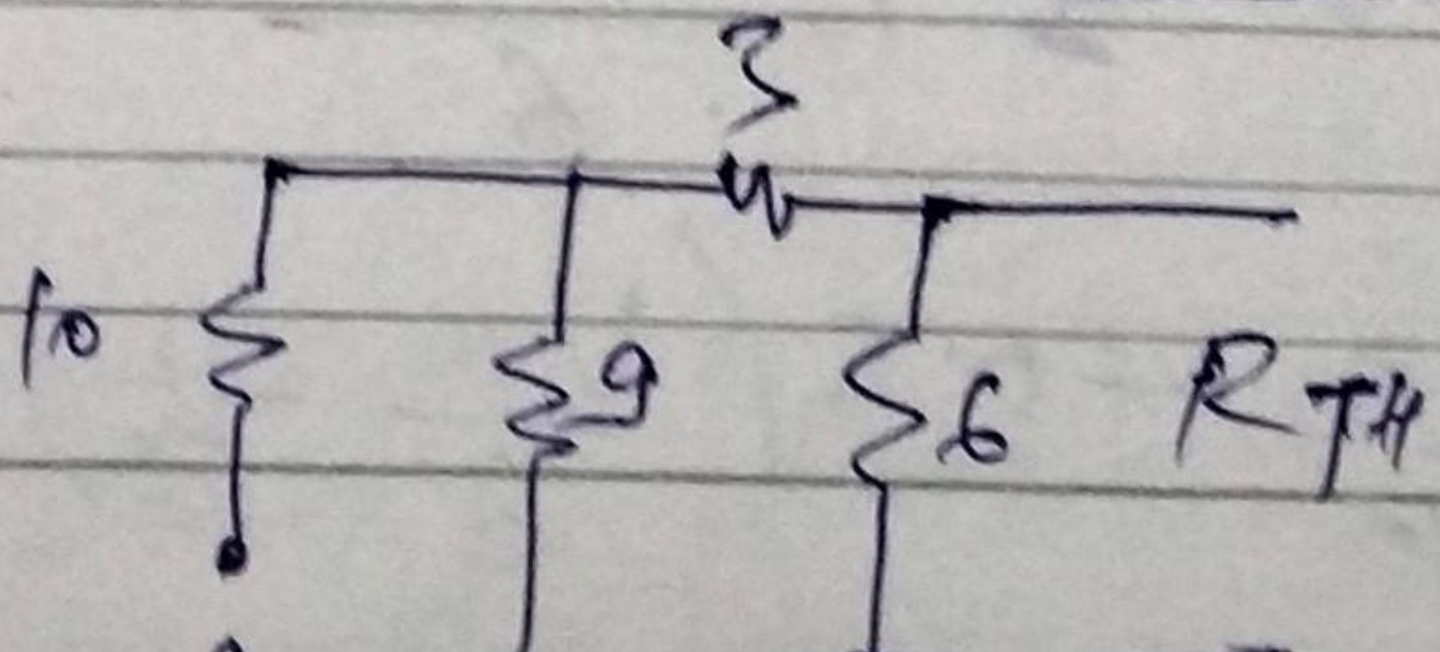
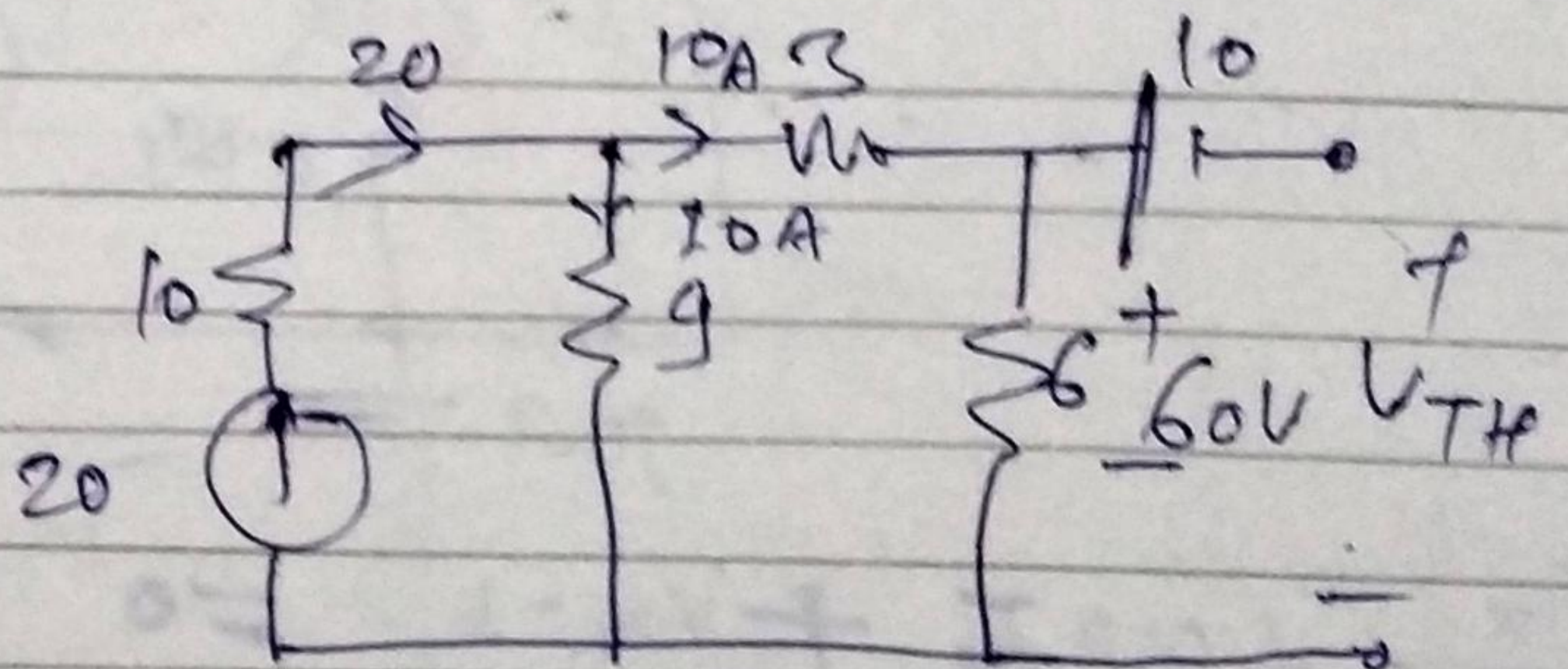


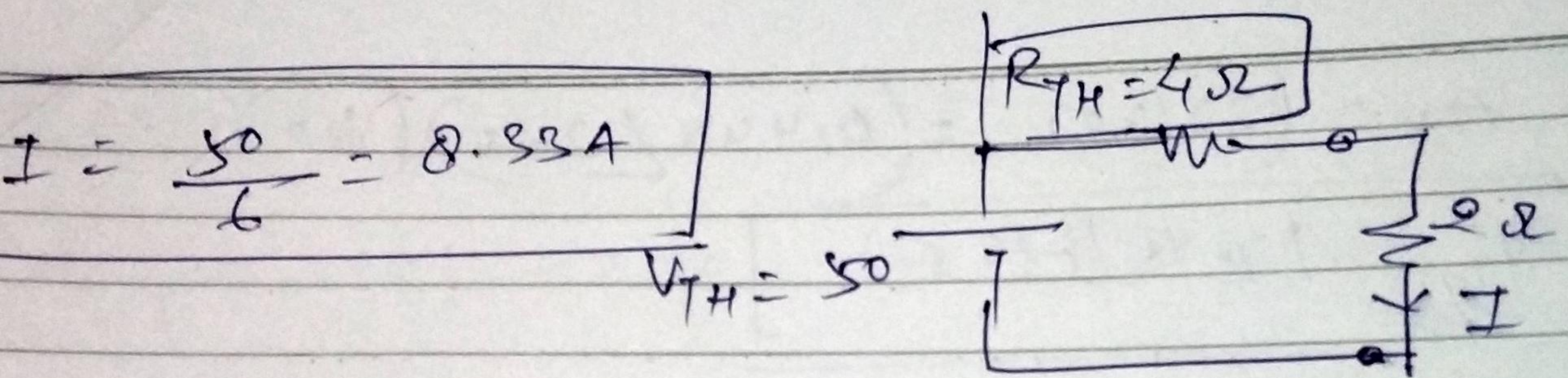

NORTON'S THEOREM :-


→ A two terminal N/W $'N_A'$ containing linear, Bilinear element and independent sources is equivalent to a ~~simple~~ ~~simple~~ N/W containing an independent current source $'I_N'$ in parallel with a Resistance $'R_N'$.

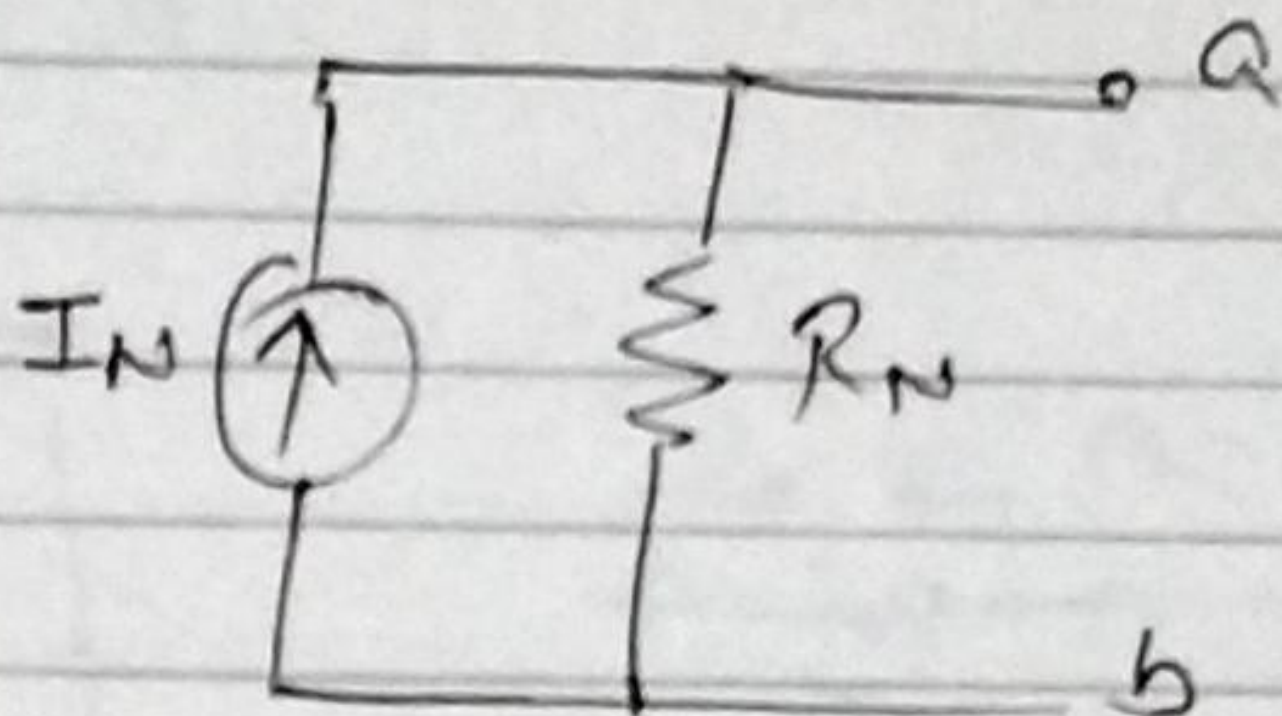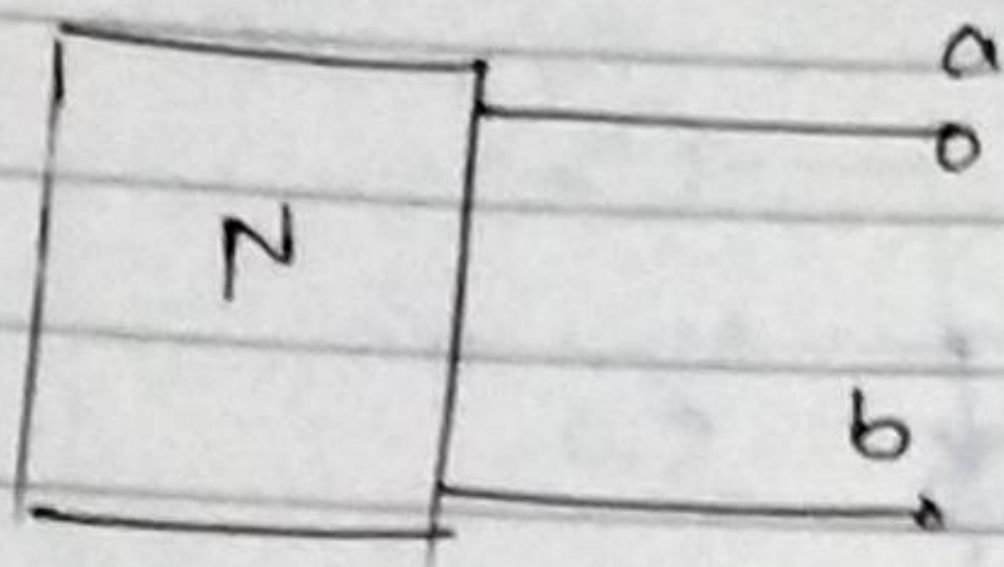→ Source current is a S.C. current across ' N_A ' and ' R_N ' is the resistance looking into the terminals after deactivating all independent sources in the N/W ' N_A '.



Ques :-


Find the current in 5Ω by using Norton's theorem.

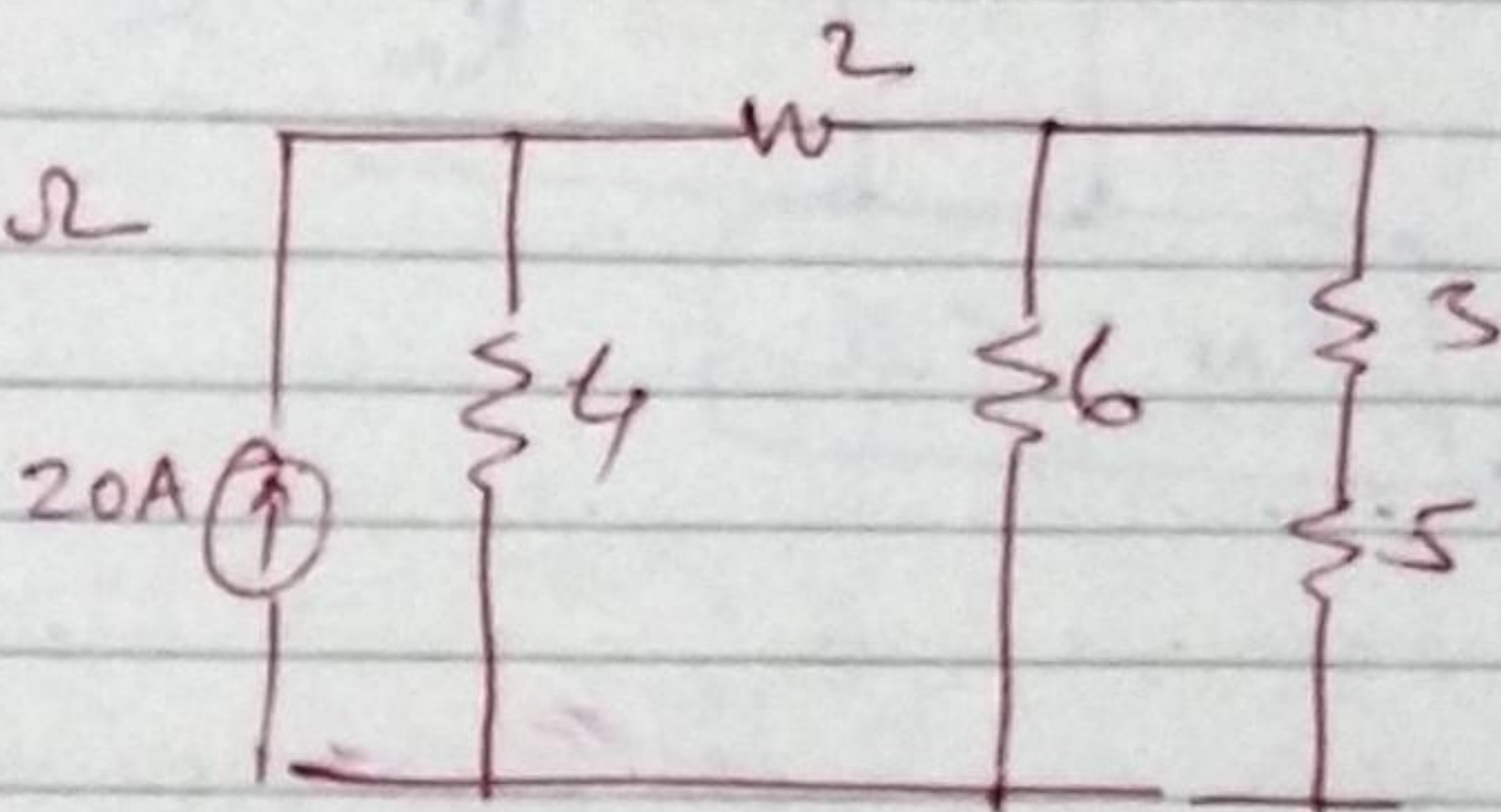

Case 1:- I_N


$$I_N = 10 \times \frac{6}{2+6}$$

$$I_N = \frac{20}{3} \text{ A}$$

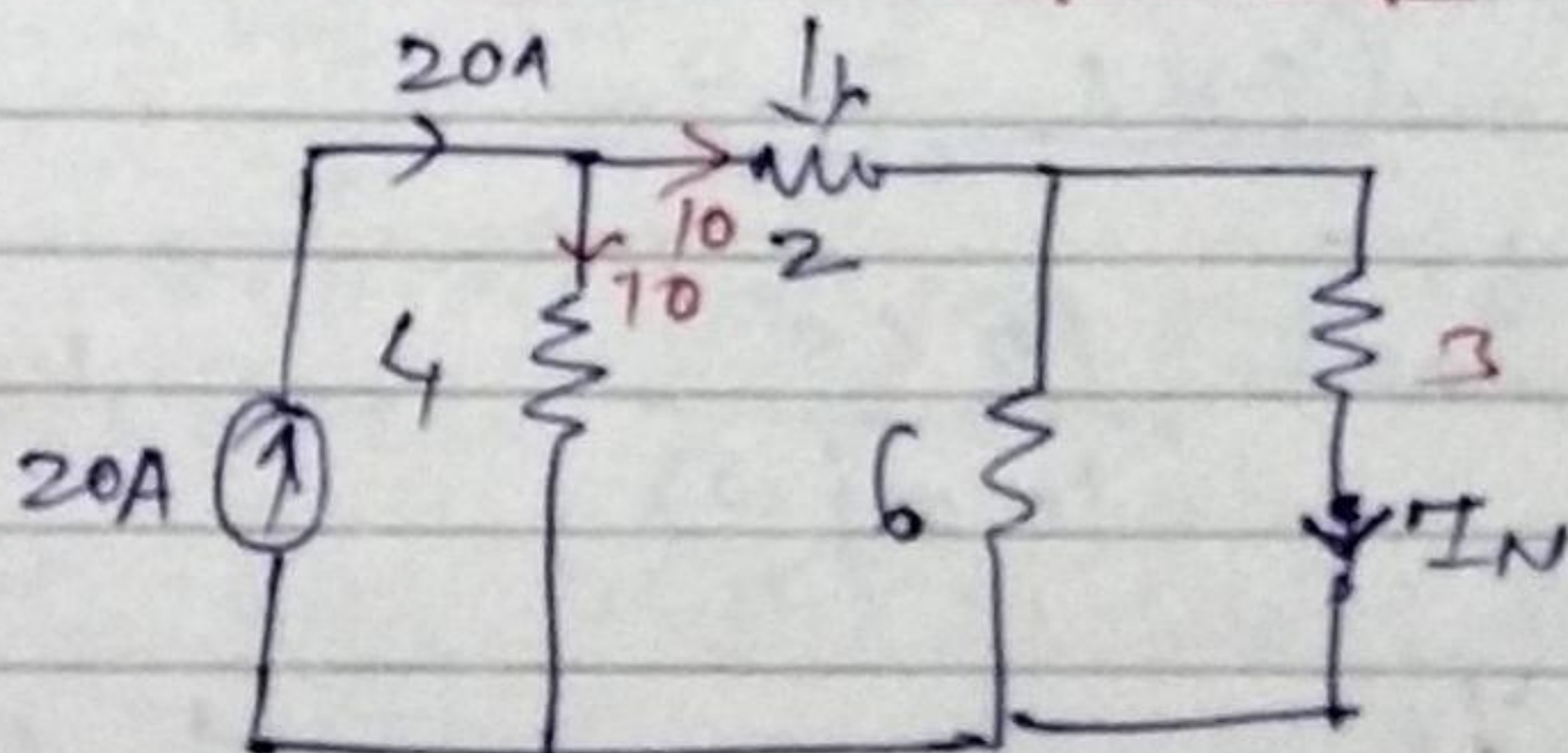


Case 2:- R_N

$$R_N = 6\Omega$$


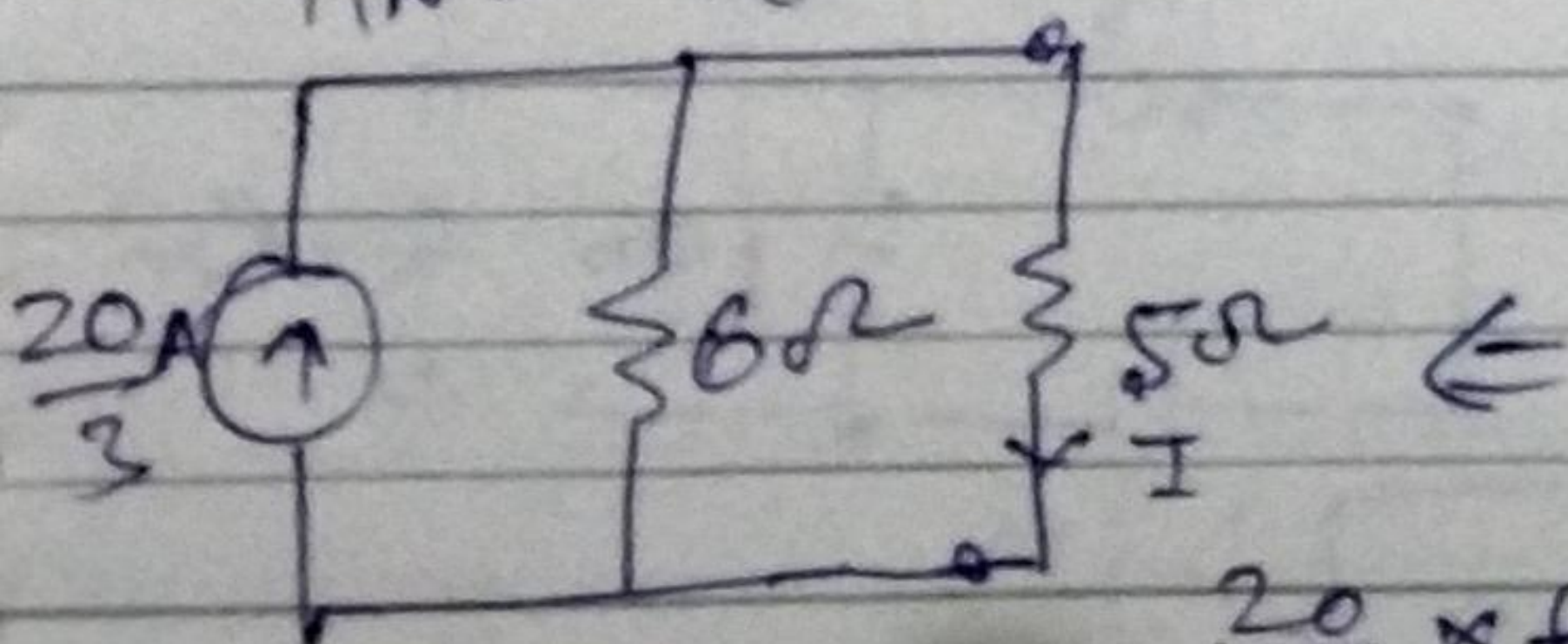

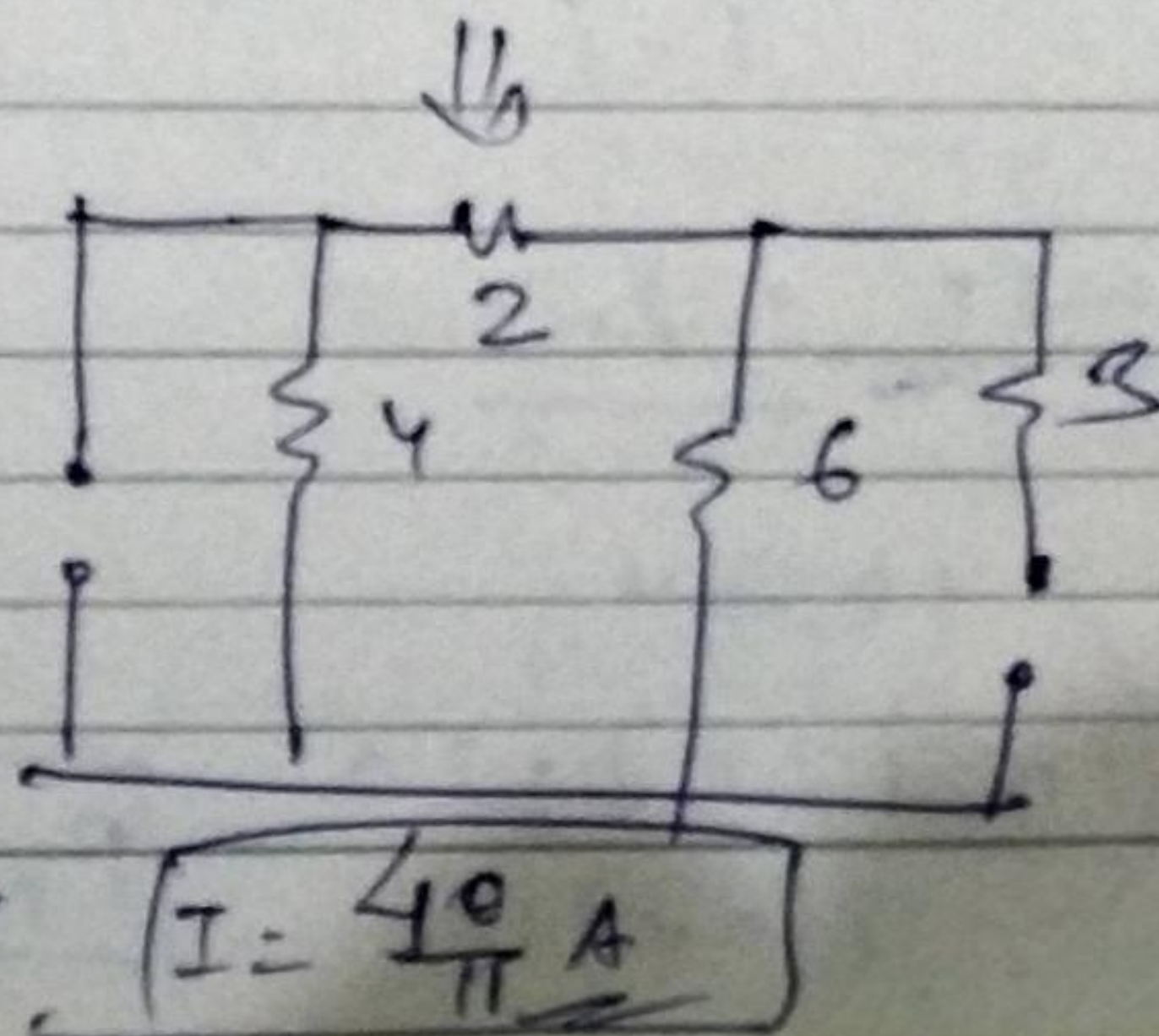
$$I = \frac{\frac{20}{3} \times 6}{2+6}$$






$$I = \frac{40}{11} \text{ A}$$

Source Transformation :-

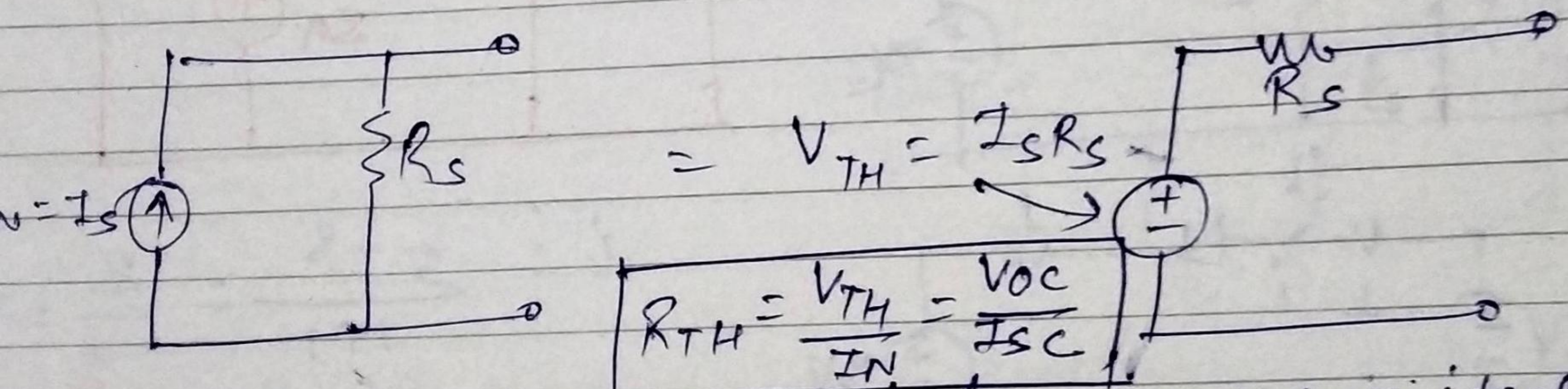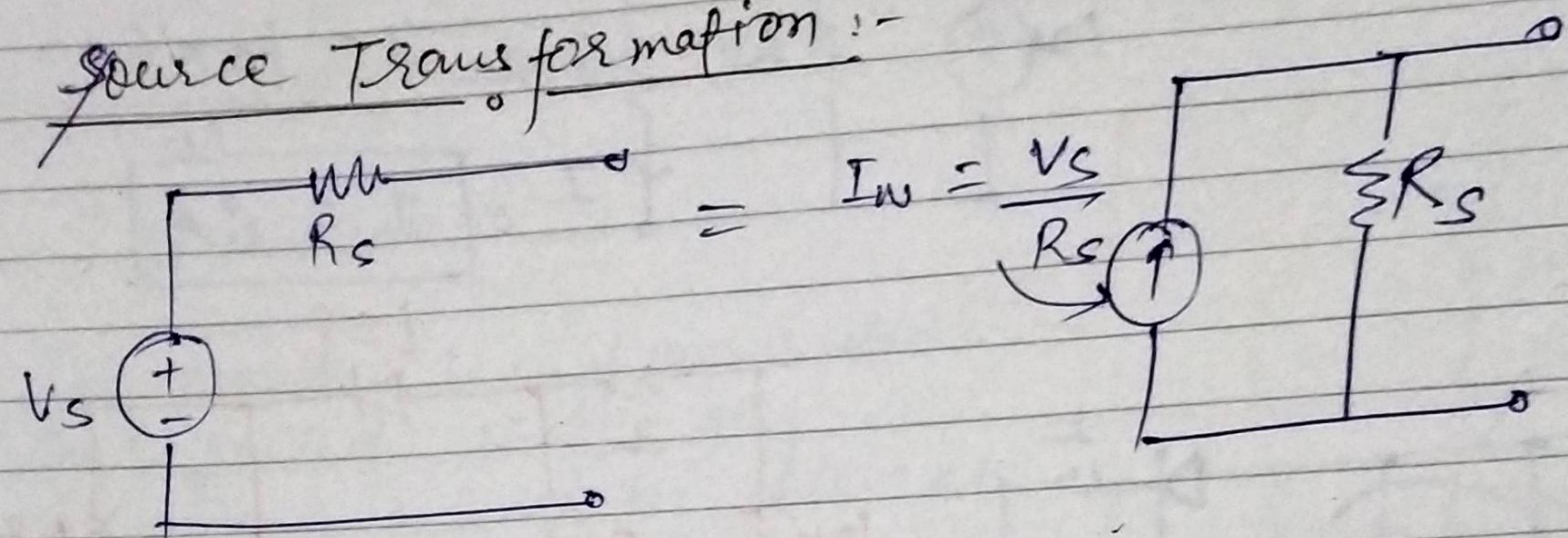

* applicable only for practical sources bcz ideal sources have zero internal resistances.

Ques:-

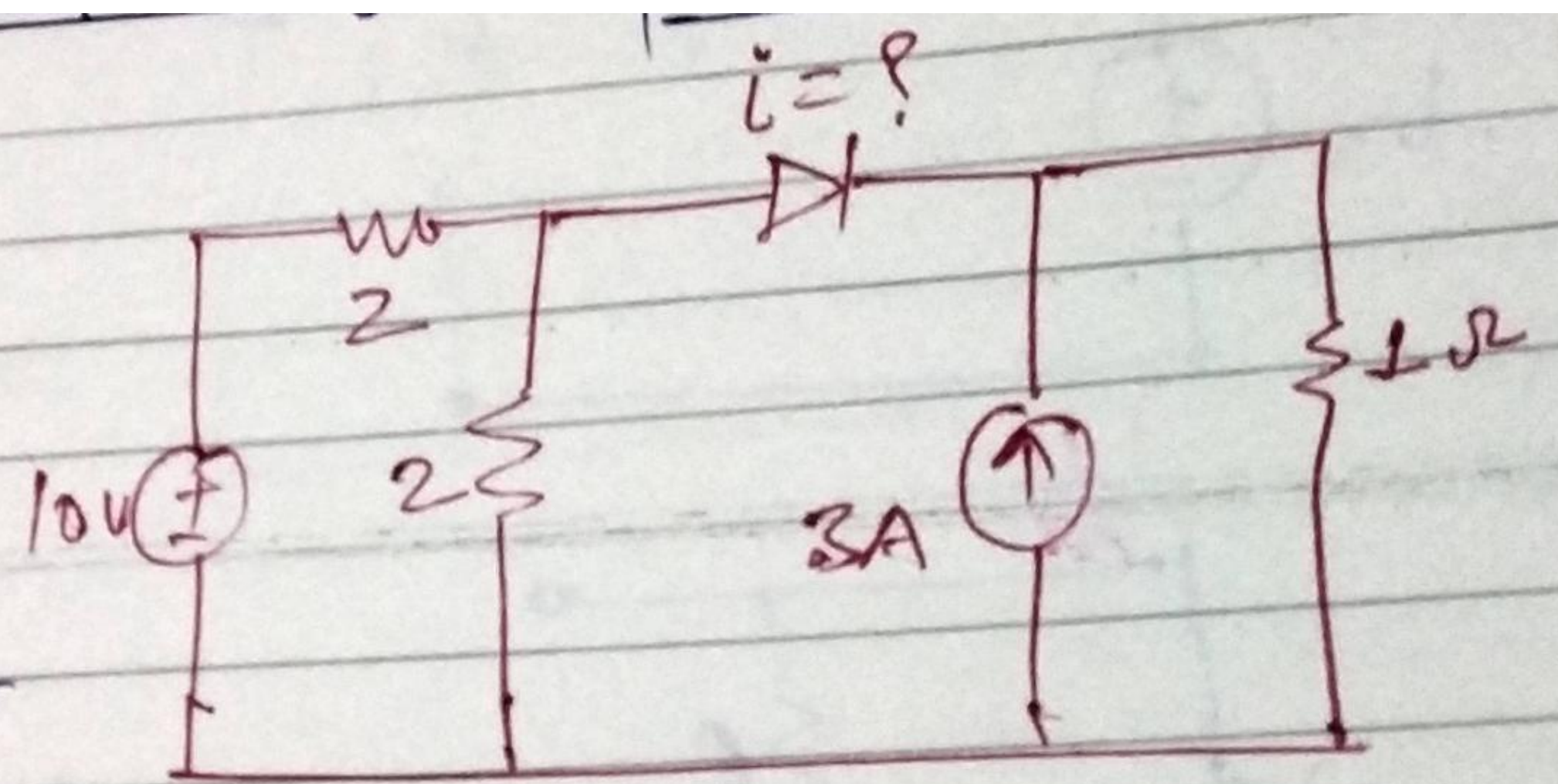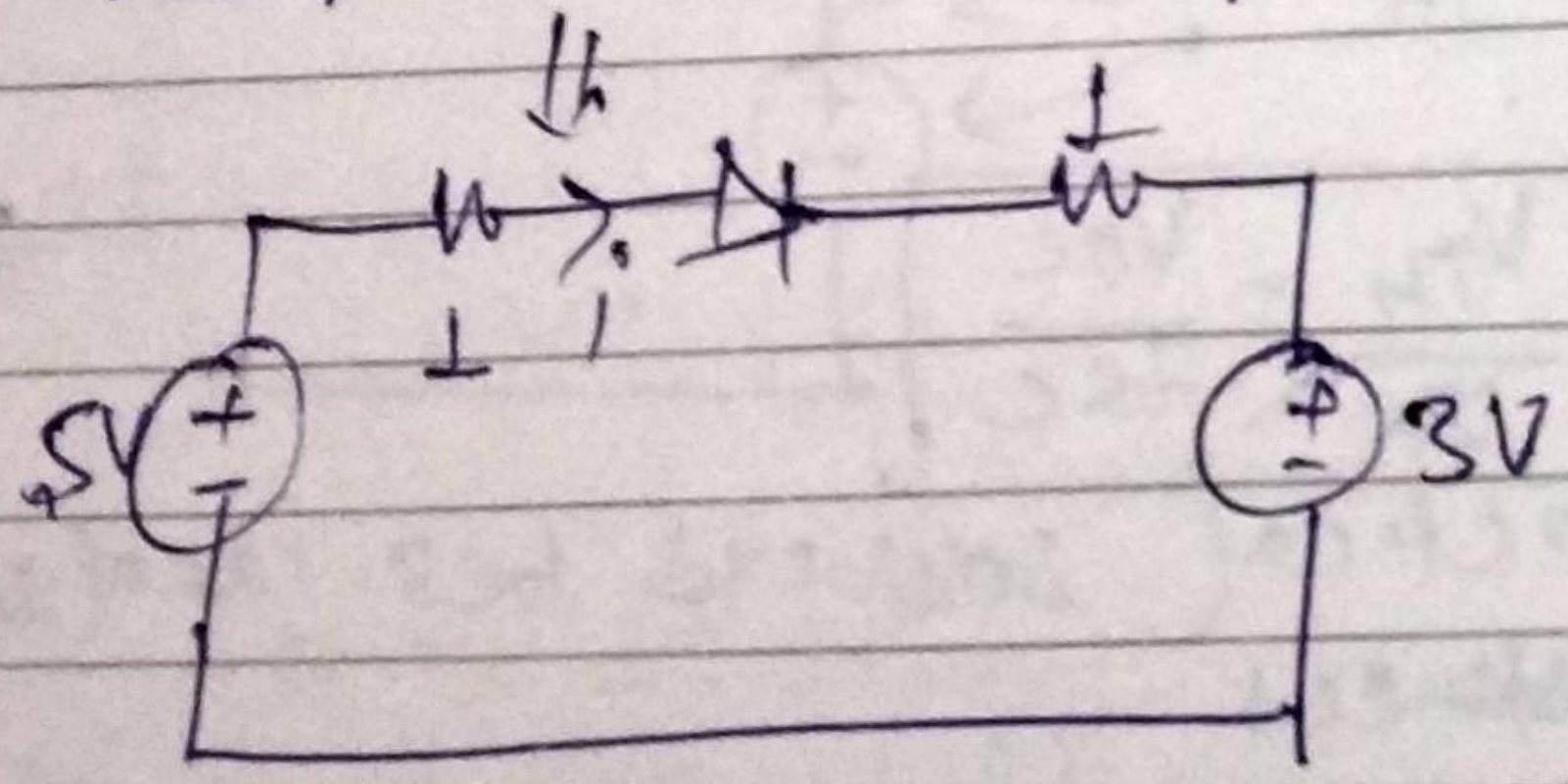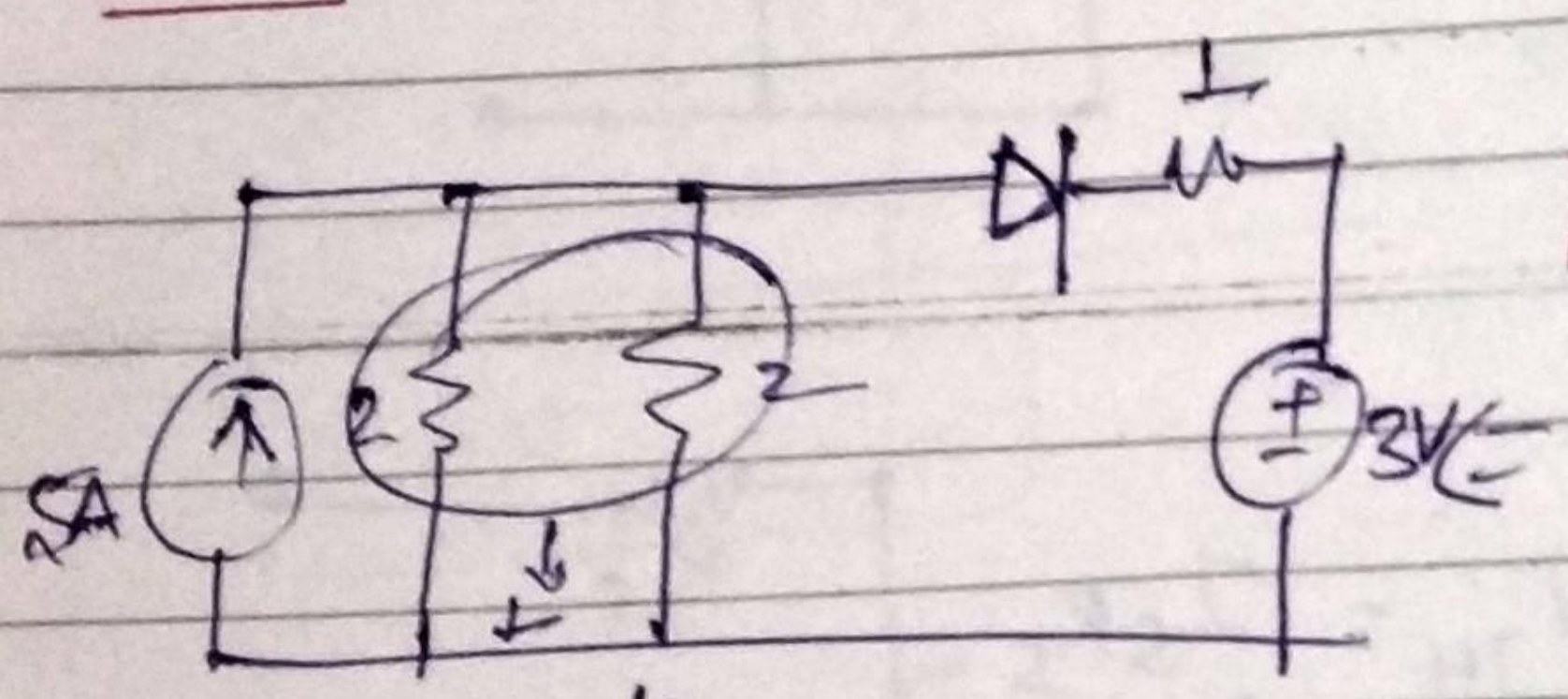


$$i = \frac{5 - 3}{1 + 1} = \frac{2}{2} = 1A$$

Maximum power Transfer Theorem:-

$$I = \frac{V_{TH}}{(R_{TH} + R_L)}$$

$$P = I^2 R_L$$
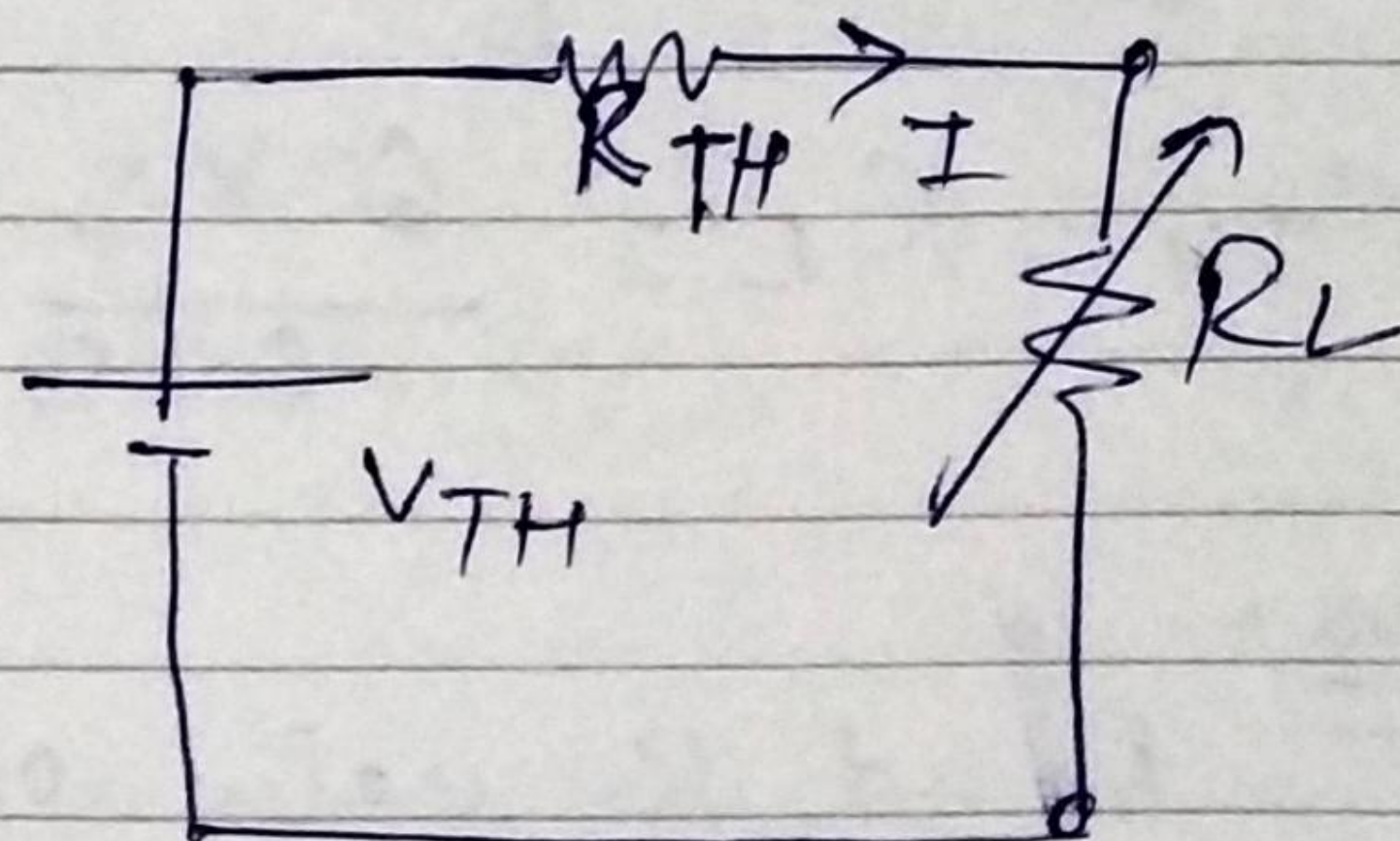
$$P = \left(\frac{V_{TH}}{R_{TH} + R_L} \right)^2 \cdot R_L$$



$$\frac{dP}{dR_L} = V_{TH}^2 \left[\frac{(R_{TH} + R_L)^2 - R_L \cdot 2(R_{TH} + R_L)}{(R_{TH} + R_L)^4} \right] = 0$$




$$R_{TH} + R_L - 2R_L = 0$$

$$R_{TH} = R_L$$

$$P_{max} = \frac{V_{TH}^2}{(R_{TH} + R_{TH})^2} \cdot R_{TH}$$

$$P_{max} = \frac{V_{TH}^2}{4 R_{TH}}$$

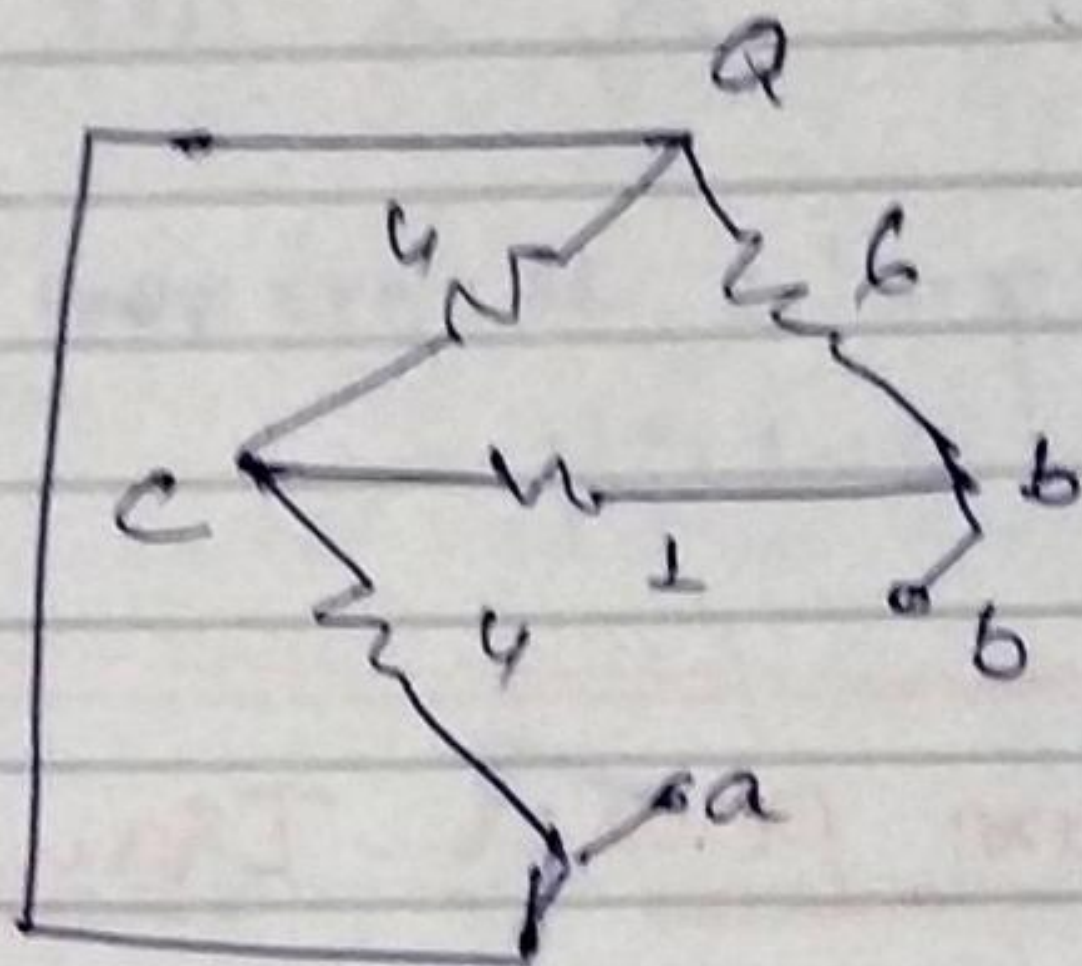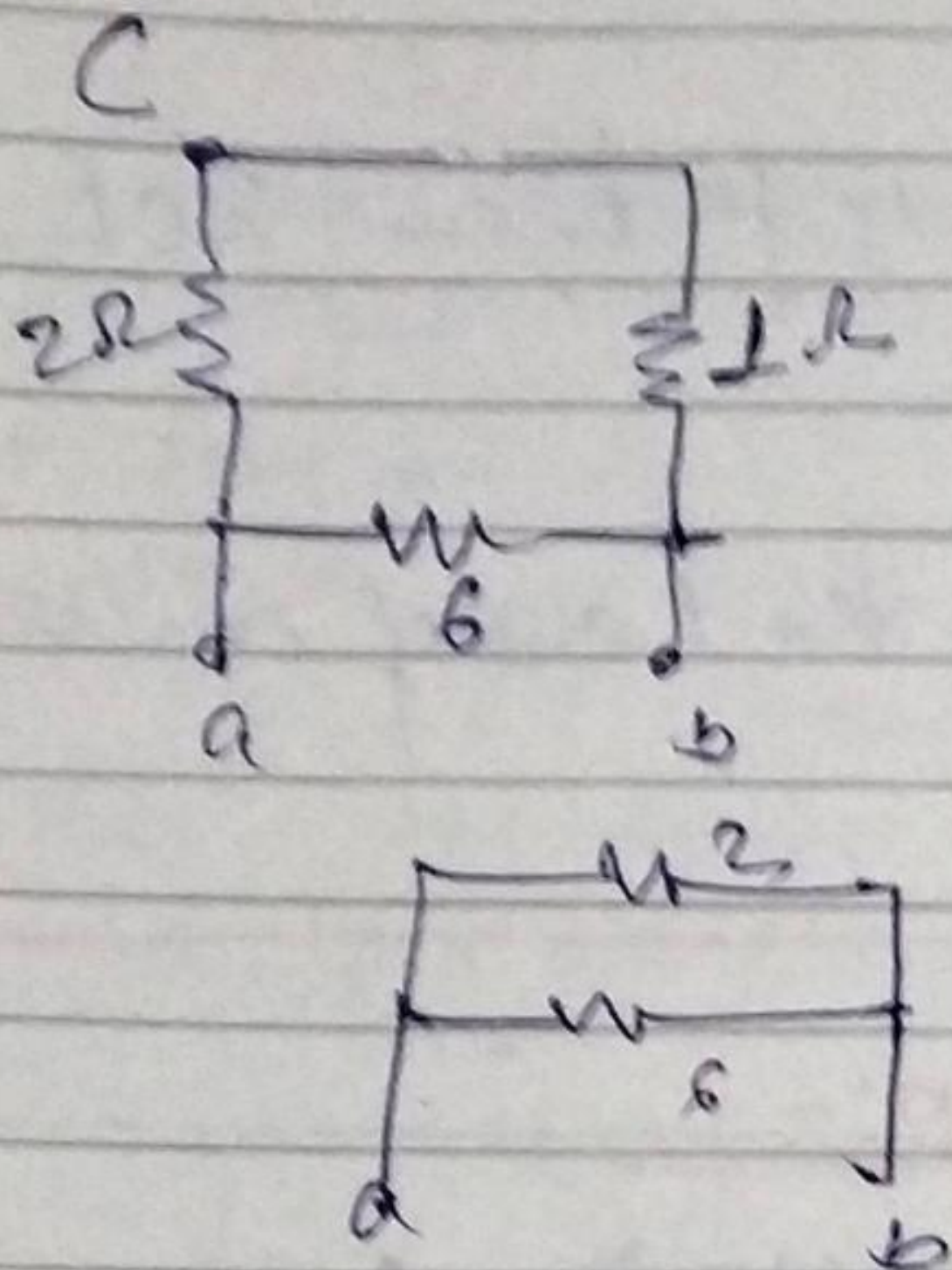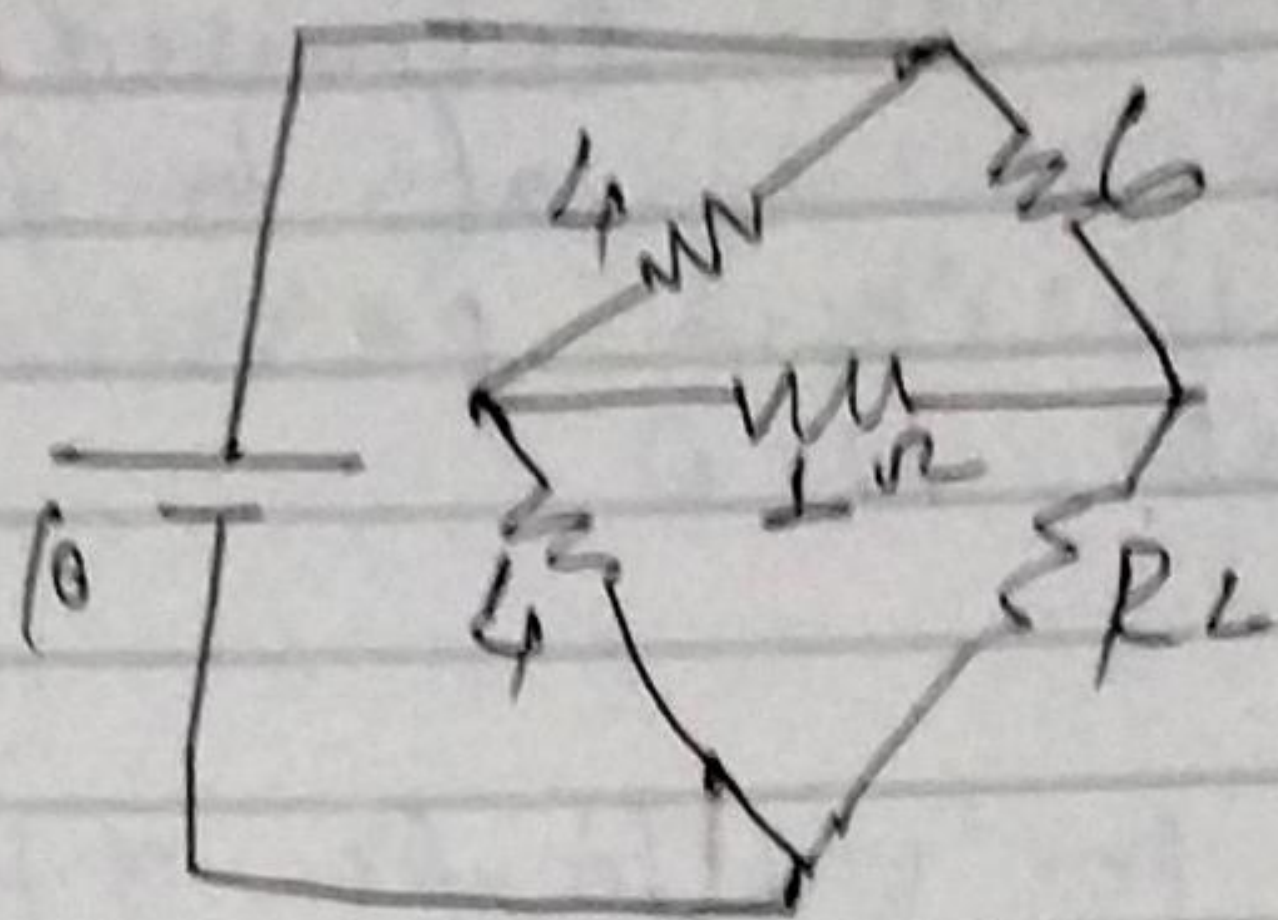
Ques. for what value of R_L max power is transferred to it.



$$R_{TH} = R_L = \frac{6 \times 3}{6 + 3} = \underline{\underline{2\Omega}}$$


Ques.

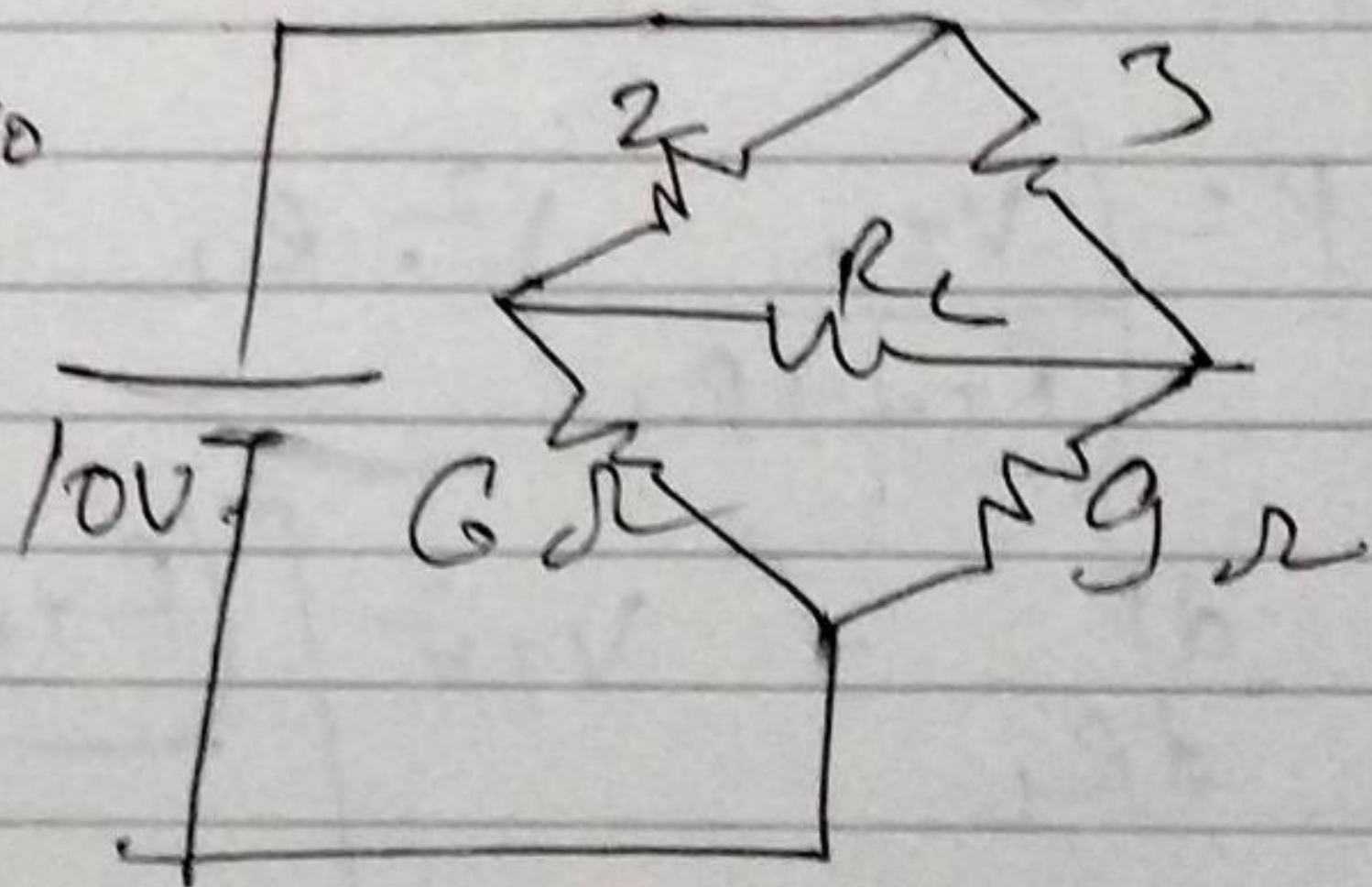Find the value of R_L so that the max power can be transferred and max power.



As the bridge is balanced
 \therefore No current is flowing through R_L and hence power dissipation will be zero.

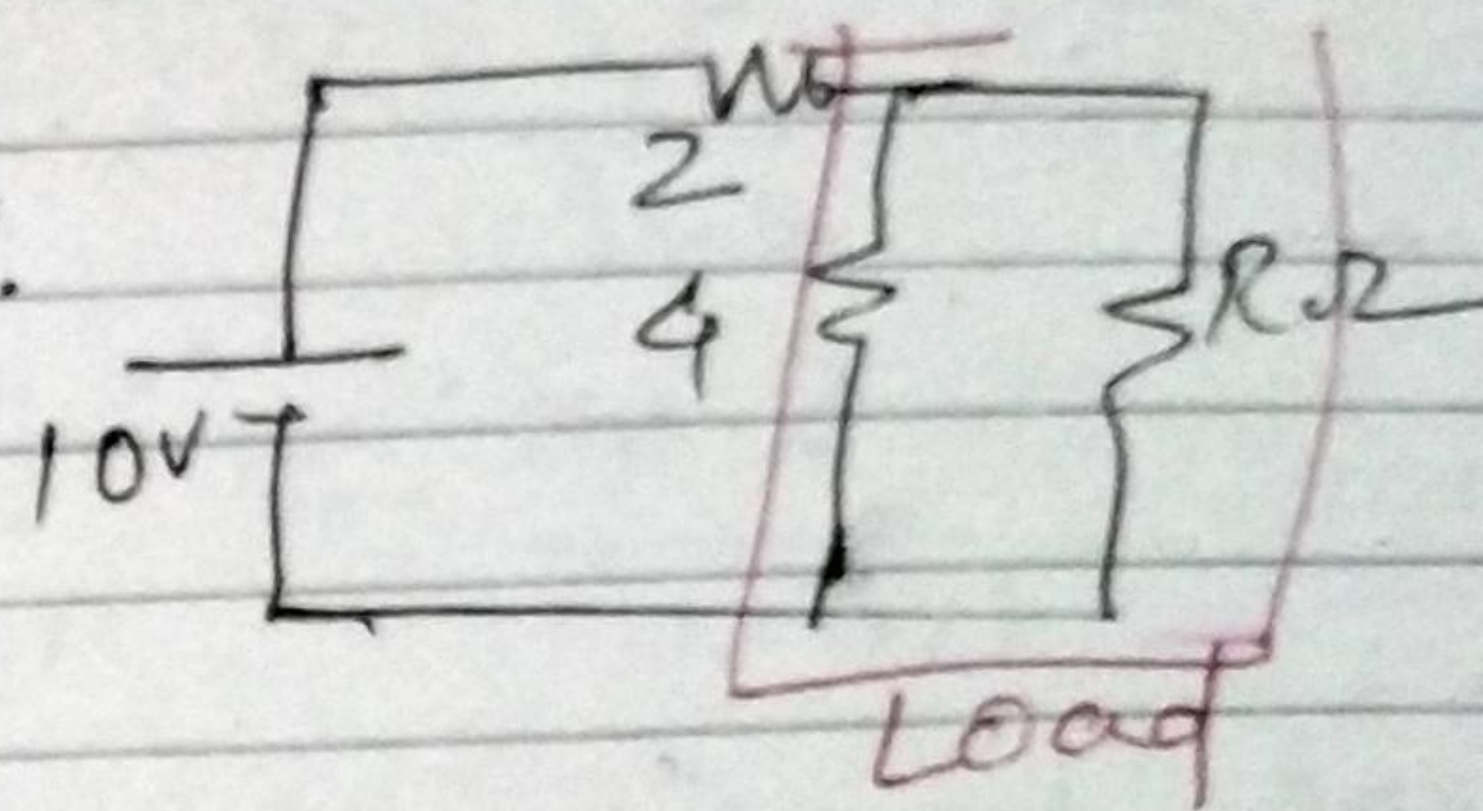Find the value of R so that
max power can be transferred.



$$R_L = R_{TH}$$

$$(4 \parallel R) = 2$$

$$\frac{4 \times R}{4 + R} = 2$$

$$R = 4\Omega$$